



ANALOG ELETRONICS

LECTURE 1:

BIPOLAR JUNCTION TRANSISTOR (BJT)

OUTLINE

- Introduction
- BJT construction
- Naming of BJT terminals
- Basic BJT Operation
- BJT Operating Modes
- Transistor Connection
- The BJT as an Amplifier



INTRODUCTION

- The transistor was invented in 1948 by J. Bardeen and W.H. Brattain of Bell Telephone Laboratories, U.S.A.;
 - The **word Transistor** comes from the **words transfer and resistor**,
 - Because an electrical current in a **transistor** is transferred across a resistor, a two-terminal component of electronics.
 - The device logically belongs in the **varistor family**, and has the **transconductance** or transfer impedance of a device having gain.
- 

INTRODUCTION

- Two basic types of transistors are the bipolar junction transistor (**BJT**), which we will begin to study in this lecture, and the field-effect transistor (**FET**) which we will cover in lecture 4.
- The **BJT** is used in two broad areas;
 - As a linear amplifier to boost or amplify an electrical signal
 - As an electronic switch.




CONSTRUCTION

- The Bipolar Junction Transistor is a **three-layer semiconductor** device consisting of either **two n-** and **one p-type** layers of material or **two p-** and **one n-type** layers of material.
- The term **bipolar** refers to the use of both holes and electrons as current carriers in the transistor structure.
- Based on its construction, a bipolar junction transistor can be classified into two types:
 - **p-n-p transistor**
 - **n-p-n transistor**




CONSTRUCTION

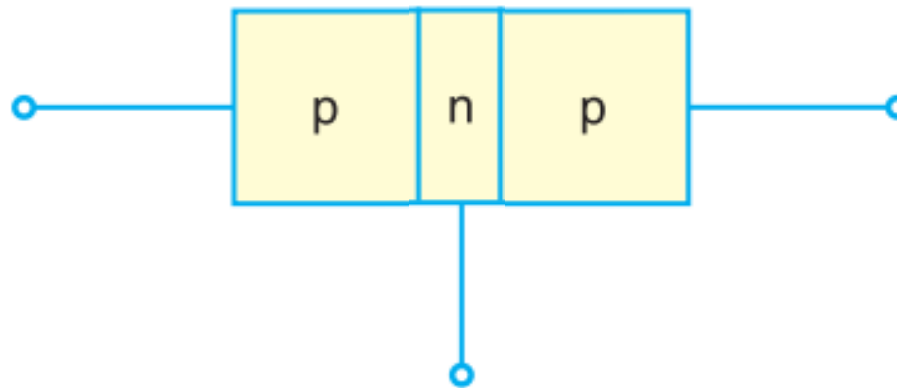- A junction transistor consists of a silicon (or germanium) crystal in which a layer of **n-type** silicon is sandwiched between two layers of **p-type** silicon, can be referred as a **p-n-p transistor**.



CONSTRUCTION

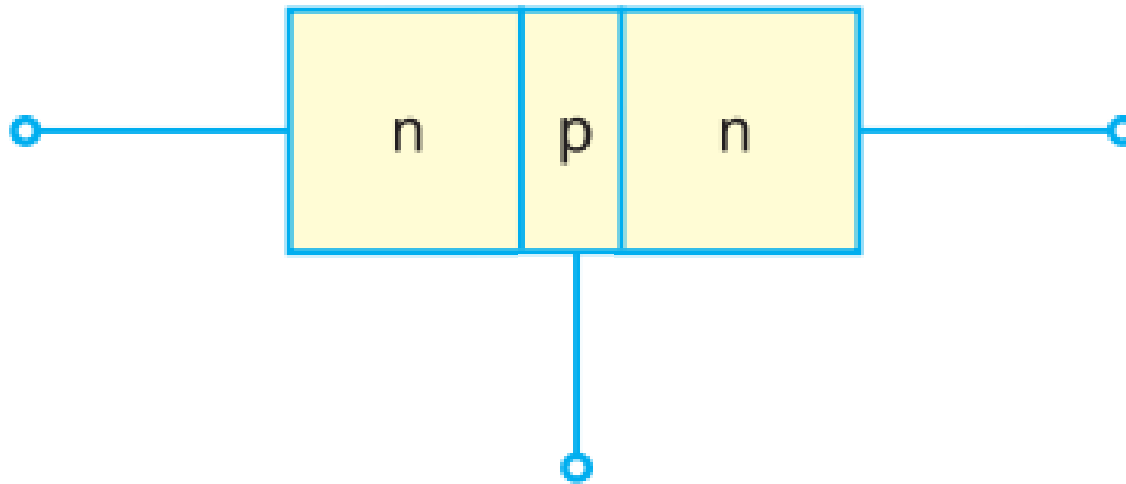- Alternatively, a junction transistor consists of a silicon (or germanium) crystal in which a layer of **p-type** silicon is sandwiched between two layers of **n-type** silicon, can be referred as a **n-p-n transistor**.



CONSTRUCTION

- In each type of transistor, the following points may be noted :
 - (i) These are two **pn junctions**. One junction is **forward biased** and the other is **reverse biased**.
 - The forward biased junction has a **low resistance** path whereas
 - A reverse biased junction has a **high resistance** path.
 - The weak signal is introduced in the low resistance circuit and output is taken from the high resistance circuit.
 - Therefore, a transistor may be regarded as a combination of two diodes connected back to back.




CONSTRUCTION

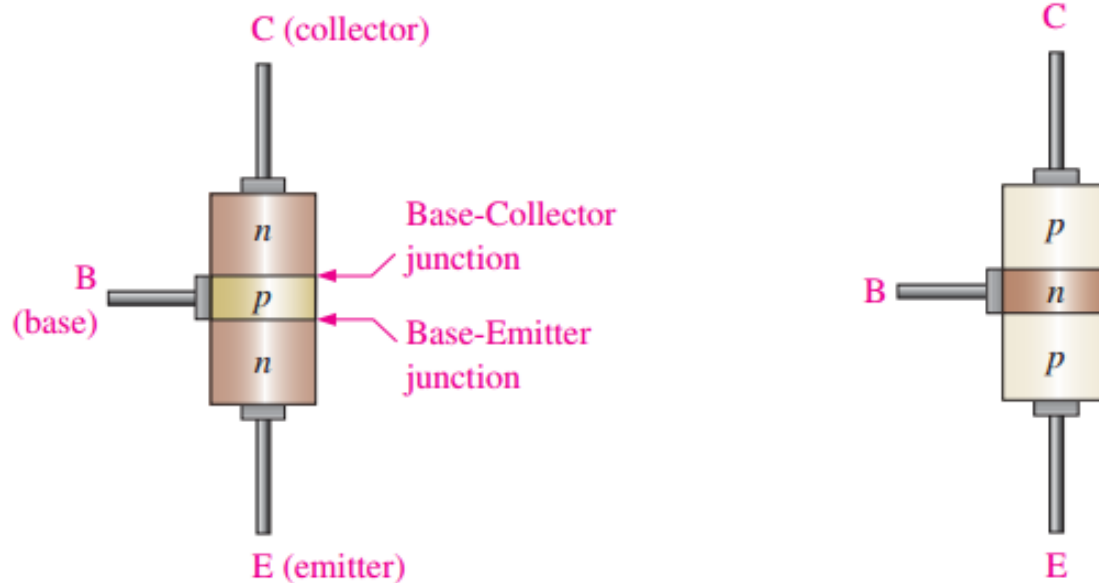- (ii) There are **three terminals**, one taken from each type of semiconductor.
- (iii) The **middle section** is a **very thin** layer. This is the most important factor in the function of a transistor.





NAMING OF TRANSISTOR TERMINALS

- The three layer of transistor are **Emitter** (E), **Base** (B) and **Collector** (C).



- The base region is **lightly doped** and **very thin** compared to the **heavily doped emitter** and the **moderately doped collector** regions.

NAMING OF TRANSISTOR TERMINALS

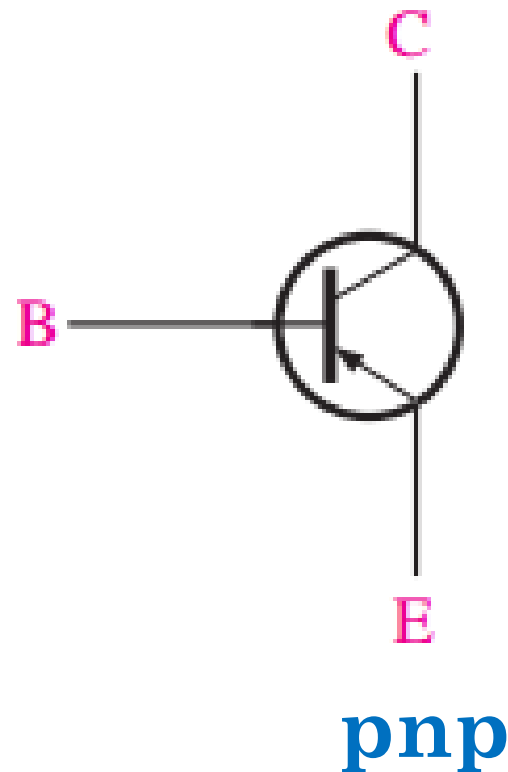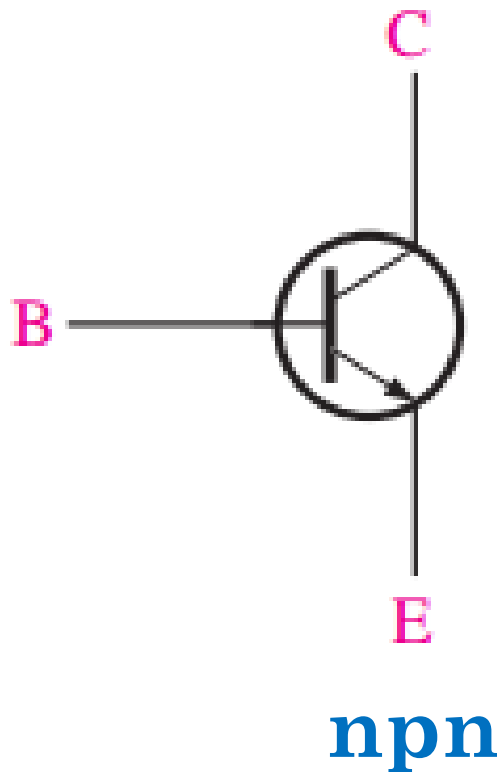

Schematic symbols for the **nnp** and **pnp** bipolar
junction transistors

NAMING OF TRANSISTOR TERMINALS

1) **Emitter:**

- The section of one side that supplies carriers is called emitter.
- Emitter is always **forward biased** with respect to base so it can supply carriers.
- For “**npn transistor**” emitter supply **holes** to its junction.
- For “**pnp transistor**” emitter supply **electrons** to its junction.



NAMING OF TRANSISTOR TERMINALS

2) Collector:



- The section on the other side that collects carrier is called collector.
- The collector is always **reversed biased** with respect to base.
- For “**nnp transistor**” collector receives **holes** to its junction.
- For “**pnnp transistor**” collector receives **electrons** to its junction.



NAMING OF TRANSISTOR TERMINALS

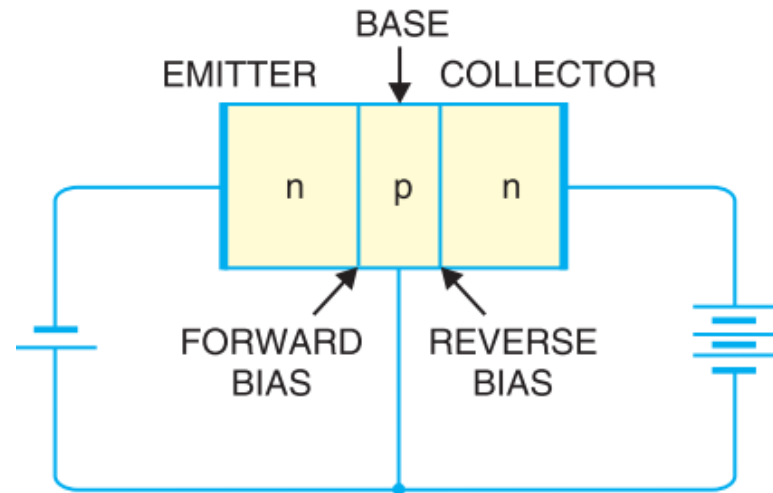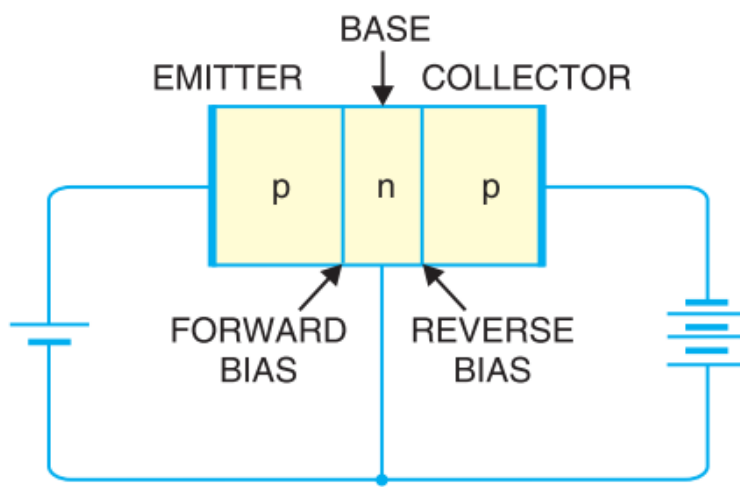3) **Base:**

- The middle section which forms two pn junction between emitter and collector is called Base.



SOME IMPORTANT FACTORS TO BE REMEMBERED


- The transistor has three region named **emitter**, **base** and **collector**.
 - The Base is much **thinner** than other region.
 - Emitter is **heavily doped** so it can inject large amount of carriers into the base.
 - Base is **lightly doped** so it can pass most of the carrier to the collector.
 - Collector is **moderately doped**.
- 

SOME IMPORTANT FACTORS TO BE REMEMBERED

- The junction between emitter and base is called **emitter-base junction**(emitter diode) and junction between base and collector is called **collector-base junction**(collector diode).
 - The emitter diode is always **forward biased** and collector diode is **reverse biased**.
 - The resistance of emitter diode is **very small**(forward) and resistance of collector diode is **high**(reverse).
- 

BASIC BJT OPERATION

1) Working of npn transistor:

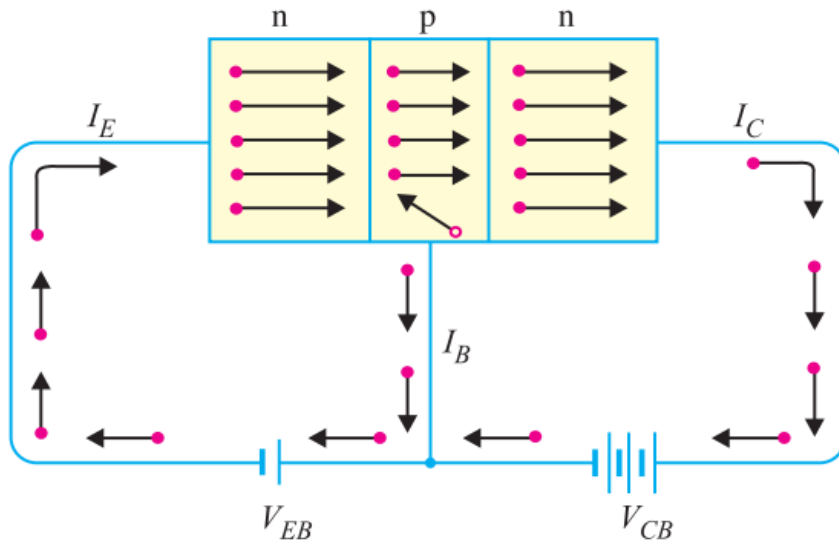

- Forward bias is applied to emitter base junction and reverse bias is applied to collector base junction.

- The forward bias causes the electrons in the n-type emitter to flow towards the base.
- This constitute emitter current, I_E

BASIC BJT OPERATION

1) Working of npn transistor:


- As these electrons flow through the p-type base, they tend to combine with holes.
- As the base is lightly doped and very thin, therefore, only a few electrons (less than 5%) combine with holes to constitute base current I_B
- The remainder (more than 95%) cross over into the collector region to constitute collector current I_C .
- Thus;

$$I_E = I_B + I_C$$



BASIC BJT OPERATION

2) Working of **pn**p transistor:

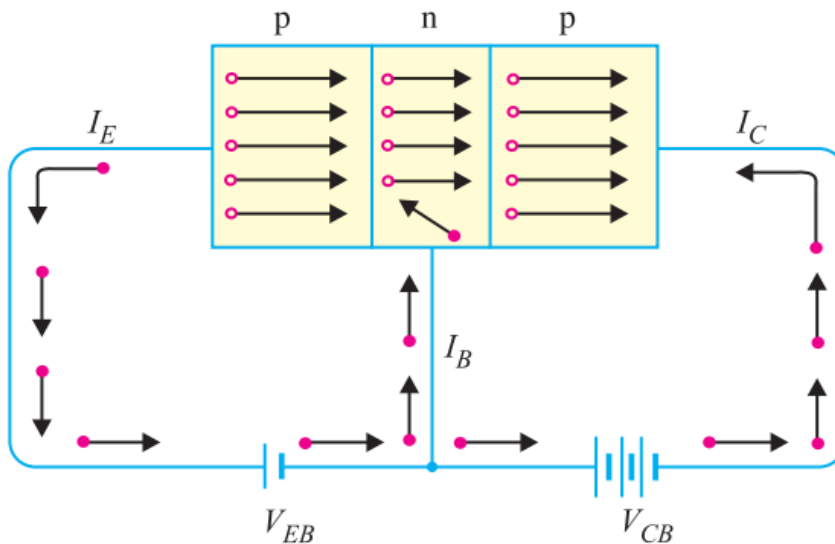

- Forward bias is applied to emitter base junction and reverse bias is applied to collector base junction.

- The forward bias causes the holes in the p-type emitter to flow towards the base.
- This constitute emitter current, I_E

BASIC BJT OPERATION

2) Working of **pnp transistor**:

- As these holes cross into n-type base, they tend to combine with the electrons.
- As the base is lightly doped and very thin, therefore, only a few holes (less than 5%) combine with the electrons.
- The remainder (more than 95%) cross into the collector region to constitute collector current I_C .
- It may be noted that current conduction within pnp transistor is by **holes**.



BJT OPERATING MODES

- Active Mode;

- Base-Emitter junction is forward
- Base-Collector junction is reverse biased.

- Saturation Mode;

- Base-Emitter junction is forward
- Base-Collector junction is forward biased.

- Cut-off Mode;

- Both junctions are reverse biased.



TRANSISTOR CONNECTION

○ Transistor can be connected in a circuit in following three ways;

1) Common Base

2) Common Emitter



3) Common Collector



TRANSISTOR CONNECTION

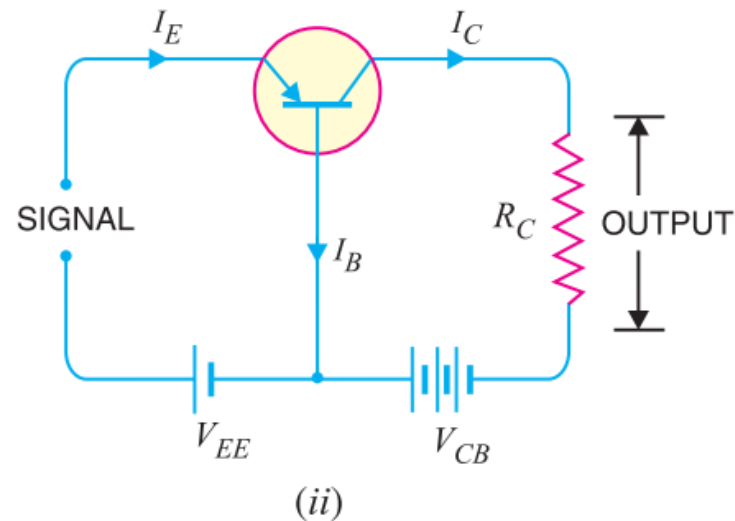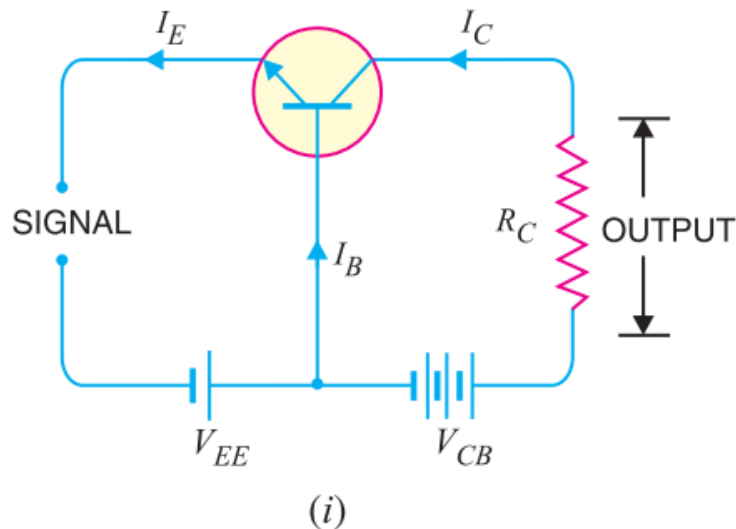1) Common Base Connection

- The base is common to both the input and output sides of the configuration.



TRANSISTOR CONNECTION

1) Common Base Connection

□ The Current amplification factor (α) :

- The ratio of change in collector current to the change in emitter current at constant V_{CB} is known as current amplification factor, α .

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \text{ at Constant } V_{CB}$$

- Practical value of α is less than unity, but in the range of 0.9 to 0.99




TRANSISTOR CONNECTION

1) Common Base Connection

❑ Characteristics of common base configuration;

❖ Input Characteristics:

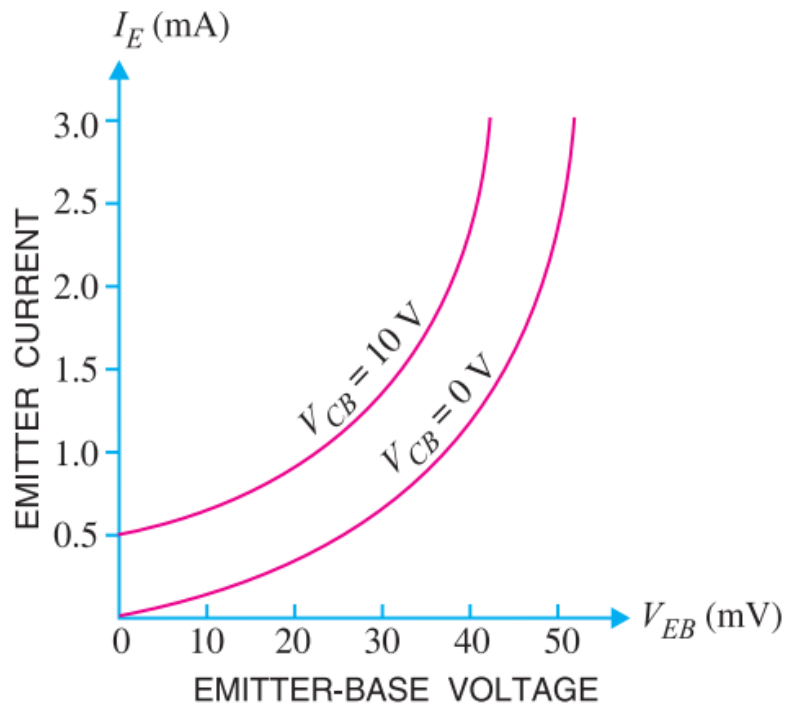


- I_E vs V_{BE} curve at constant V_{CB} is called input characteristics.
- I_E increases rapidly with V_{BE}
- It means input resistance is very small.
- I_E is almost independent of V_{CB} .

TRANSISTOR CONNECTION

1) Common Base Connection

❑ Characteristics of common base configuration;

❖ Output Characteristics:

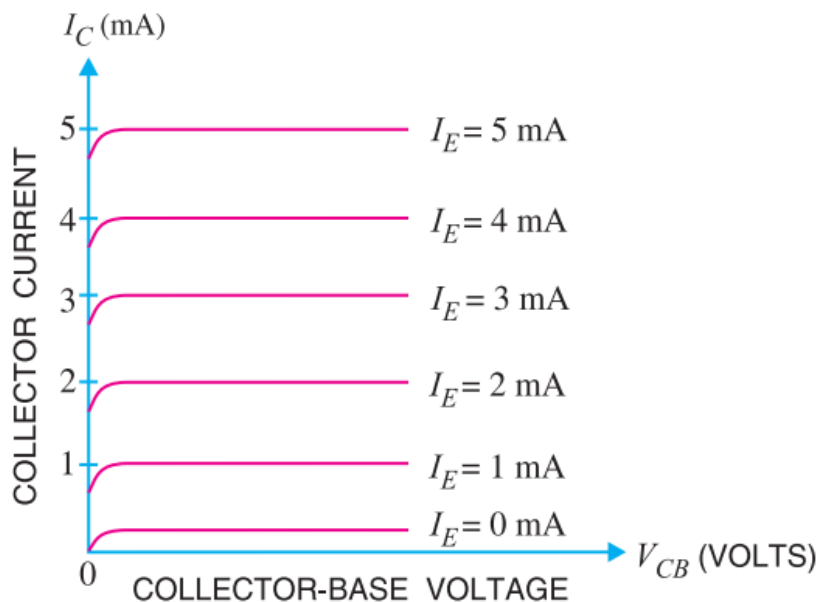

- I_C vs V_{CB} curve at constant I_E
- The I_C varies with V_{CB} only at very low voltages ($< 1V$).
- The transistor is **never** operated in this region.
- I_C varies linearly with V_{CB} , only when V_{CB} is very small.
- As, V_{CB} increases, I_C becomes constant.

TRANSISTOR CONNECTION

1) Common Base Connection

❑ Characteristics of common base configuration;

❖ Input resistance:

The ratio of change in emitter-base voltage (ΔV_{BE}) to the resulting change in emitter current (ΔI_E) at constant collector-base voltage (V_{CB})

$$\text{Input resistance, } r_i = \frac{\Delta V_{BE}}{\Delta I_E} \text{ at constant } V_{CB}$$



TRANSISTOR CONNECTION

1) Common Base Connection

❑ Characteristics of common base configuration;

❖ **Output resistance:**

The ratio of change in collector-base voltage (ΔV_{CB}) to the resulting change in collector current (ΔI_C) at constant emitter current (I_E).

$$\text{Input resistance, } r_o = \frac{\Delta V_{CB}}{\Delta I_C} \text{ at constant } I_E$$



TRANSISTOR CONNECTION

Example 1: In a common base connection, $I_E = 1\text{mA}$, $I_C = 0.95\text{mA}$. Calculate the value of I_B .

Solution:

Using the relation, $I_E = I_B + I_C$ or $1 = I_B + 0.95$

$$\therefore I_B = 1 - 0.95 = \mathbf{0.05\text{ mA}}$$

Example 2: In a common base connection, current amplification factor is 0.9. If the emitter current is 1mA, determine the value of base current.

Solution:

Here, $\alpha = 0.9$, $I_E = 1\text{mA}$

$$\text{Now } \alpha = \frac{I_C}{I_E}$$

$$\text{or } I_C = \alpha I_E = 0.9 \times 1 = \mathbf{0.9\text{ mA}}$$

$$\text{Also } I_E = I_B + I_C$$

$$\therefore \text{Base current, } I_B = I_E - I_C = 1 - 0.9 = \mathbf{0.1\text{ mA}}$$



TRANSISTOR CONNECTION

Example 3: In a common base connection, $I_C = 0.95\text{mA}$ and $I_B = 0.05\text{ mA}$. Find the value of α

Solution:

We know $I_E = I_B + I_C = 0.05 + 0.95 = 1\text{ mA}$

$\therefore$ Current amplification factor, $\alpha = \frac{I_C}{I_E} = 0.95$

Example 4: In a common base connection, $\alpha = 0.95$. The voltage drop across $2\text{ k}\Omega$ resistance which is connected in the collector is 2V . Find the base current.

Solution:


The voltage drop across $R_C (=2\text{ k}\Omega)$ is 2V .

$$I_C = \frac{2\text{ V}}{2\text{ k}\Omega} = 1\text{mA},$$

$$\text{Now, } \alpha = \frac{I_C}{I_E} \text{ or } I_E = \frac{I_C}{\alpha} = \frac{1\text{mA}}{0.95} = 1.05\text{ mA}$$

Using the relation, $I_E = I_B + I_C$ or $1.05 = I_B + 1$
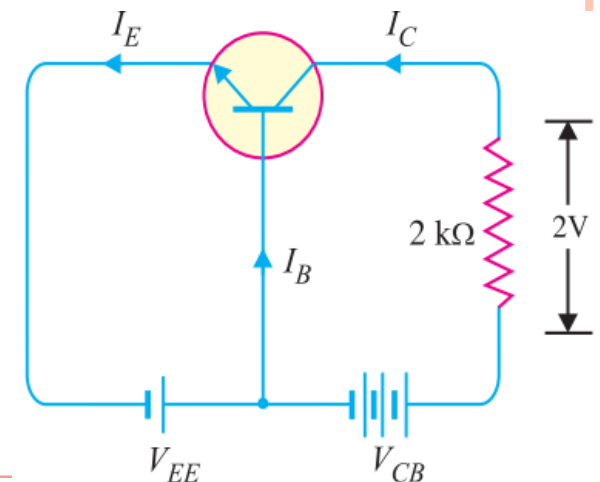
$$\therefore I_B = 1.05 - 1 = 0.05\text{ mA}$$




TRANSISTOR CONNECTION

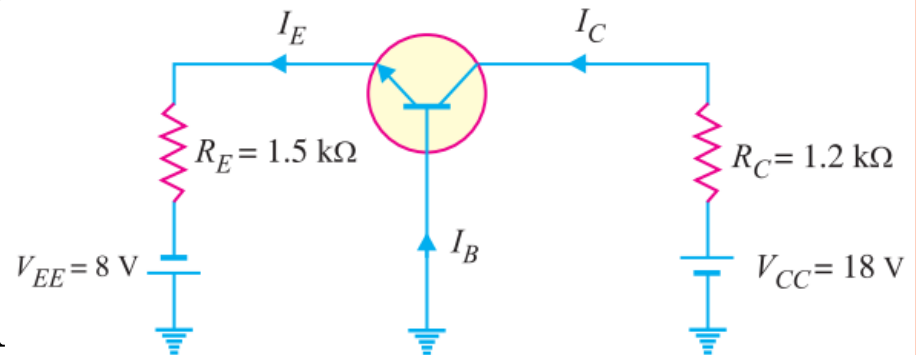Example 5: *In For the common base circuit shown in Fig below, determine I_C and V_{CB} . Assume the transistor to be of silicon.*

Solution: Since the transistor is of silicon, $V_{BE} = 0.7V$. Applying Kirchhoff's voltage law to the emitter-side loop, we get;

$$V_{EE} = I_E R_E + V_{BE}$$
$$I_E = \frac{V_{EE} - V_{BE}}{R_E} = \frac{8V - 0.7V}{1.5k} = 4.87mA$$
$$\therefore I_C \approx I_E = 4.87mA$$



Applying Kirchhoff's voltage law to the collector-side loop, we have,



$$V_{CC} = I_C R_C + V_{CB}$$

$$V_{CB} = V_{CC} - I_C R_C = 18V - 4.87mA \times 1.2k = 12.16V$$

TRANSISTOR CONNECTION

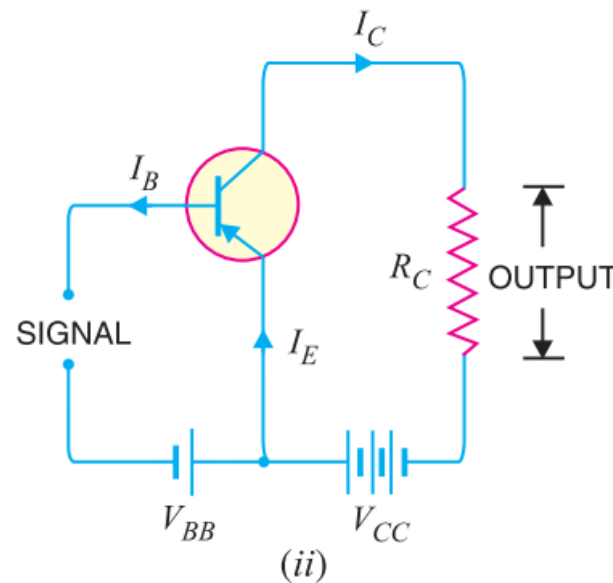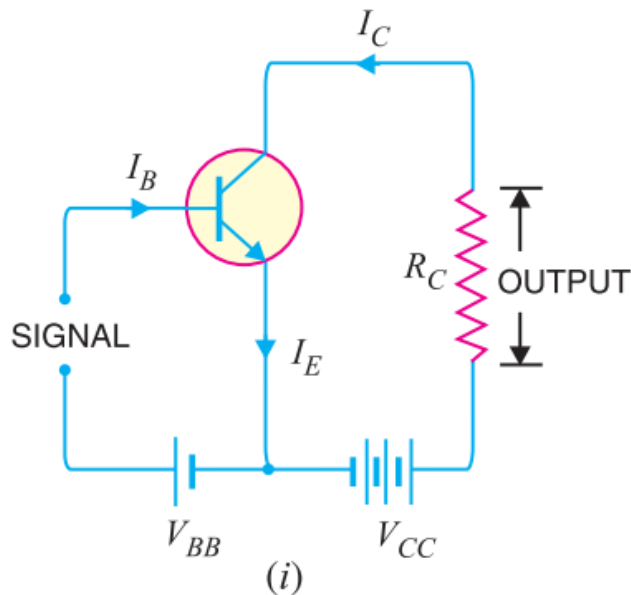2) Common Emitter Connection

- The emitter is common to both the input and output sides of the configuration.
- Input is applied between base and emitter and output is taken from the collector and emitter.



TRANSISTOR CONNECTION

2) Common Emitter Connection

□ Base current amplification factor (β):

- The ratio of change in collector current (ΔI_C) to the change in base current (ΔI_B) is known as base current amplification factor.

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

- The value of β ranges from 20 to 500.
- This type of connection is frequently used as it gives appreciable current gain as well as voltage gain.



TRANSISTOR CONNECTION

2) Common Emitter Connection

□ Relation between β and α :

$$\beta = \frac{\Delta I_C}{\Delta I_B} \text{ and } \alpha = \frac{\Delta I_C}{\Delta I_E}$$

Now

$$I_E = I_C + I_B$$

or

$$\Delta I_E = \Delta I_C + \Delta I_B$$

or

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C} = \frac{\Delta I_C / \Delta I_E}{\Delta I_E / \Delta I_E - \Delta I_C / \Delta I_E} = \frac{\alpha}{1 - \alpha}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$




TRANSISTOR CONNECTION

2) Common Emitter Connection

❑ Characteristics of common emitter configuration :

❖ Input characteristics:

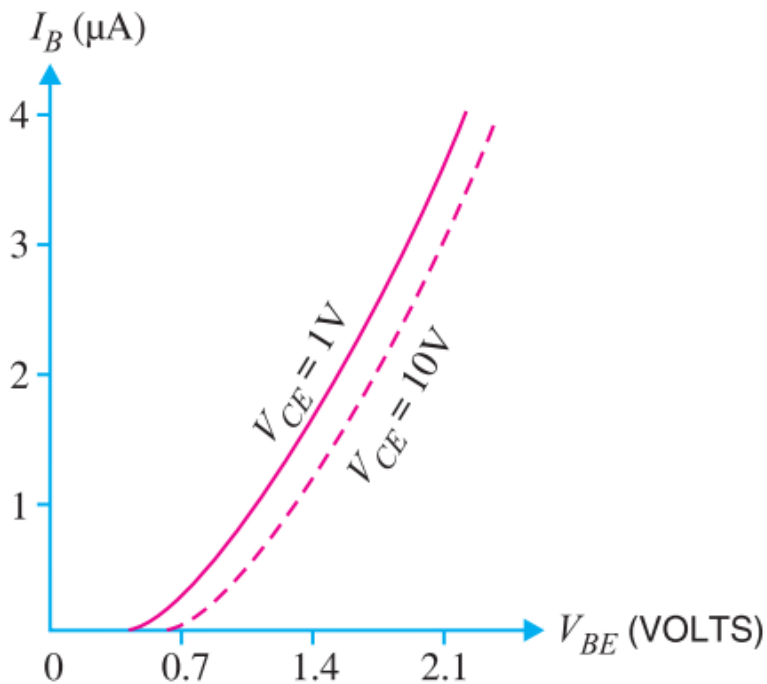


- V_{BE} vs I_B curve is called input characteristics.
- I_B increases rapidly with V_{BE} .
- It means input resistance is very small.
- I_E almost independent of V_{CE} .
- I_B is of the range of micro amps.

TRANSISTOR CONNECTION

2) Common Emitter Connection

❑ Characteristics of common emitter configuration :

❖ Output characteristics :

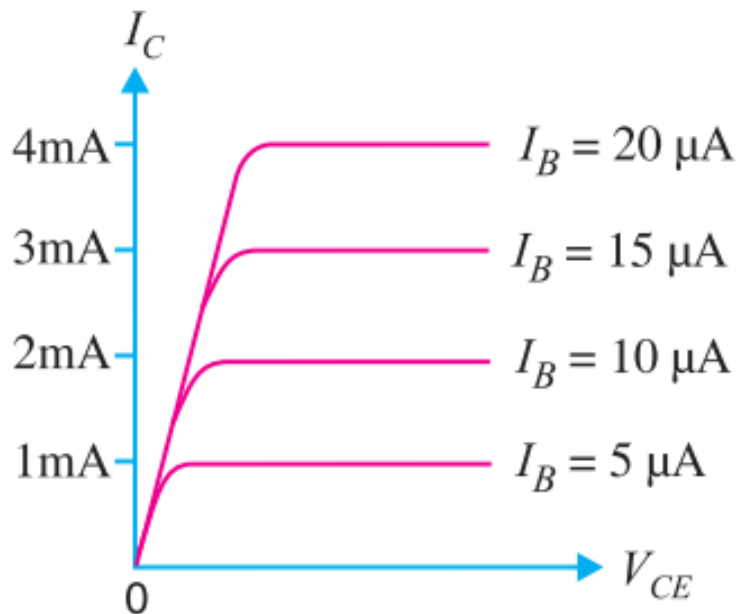

- V_{CE} vs I_C curve is called output characteristics.
- I_C varies linearly with V_{CE} , only when V_{CE} is very small.
- As, V_{CE} increases, I_C becomes constant.



TRANSISTOR CONNECTION

2) Common Emitter Connection

❑ Characteristics of common emitter configuration :

❖ Input resistance:

- The ratio of change in base-emitter voltage (ΔV_{BE}) to the change in base current (ΔI_B) at constant V_{CE} .

$$\text{Input resistance, } r_i = \frac{\Delta V_{BE}}{\Delta I_B} \text{ at constant } V_{CE}$$



TRANSISTOR CONNECTION

2) Common Emitter Connection

❑ Characteristics of common emitter configuration :

❖ **Output resistance:**

- The ratio of change in collector-emitter voltage (ΔV_{CE}) to the change in collector current (ΔI_C) at constant I_B

$$\text{Output resistance, } r_o = \frac{\Delta V_{CE}}{\Delta I_C} \text{ at constant } I_B$$



TRANSISTOR CONNECTION

Example 6:

Find the value of β if (i) $\alpha = 0.9$ (ii) $\alpha = 0.98$ (iii) $\alpha = 0.99$.

Solution:

$$(i) \quad \beta = \frac{\alpha}{1-\alpha} = \frac{0.9}{1-0.9} = 9$$

$$(ii) \quad \beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{1-0.98} = 49$$

$$(iii) \quad \beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = 99$$

Example 7:

Calculate I_E in a transistor for which $\beta = 50$ and $I_B = 20 \mu A$

Solution:

Here $\beta = 50$, $I_B = 20 \mu A = 0.02 \text{ mA}$

$$\beta = \frac{I_C}{I_B}$$

$$I_C = \beta I_B = 50 \times 0.02 \text{ mA} = 1 \text{ mA}$$

Using the relation, $I_E = I_C + I_B = 0.02 + 1 = 1.02 \text{ mA}$



TRANSISTOR CONNECTION

Example 8:

Find the arating of the transistor shown in Fig. Hence determine the value of I_C using both α and β rating of the transistor.


Solution:

$$\alpha = \frac{\beta}{1+\beta} = \frac{49}{1+49} = \mathbf{0.98}$$

The value of I_C can be found by using either α or β rating as under :

$$I_C = \alpha I_E = 0.98 \times 12 \text{ mA} = \mathbf{11.76 \text{ mA}}$$
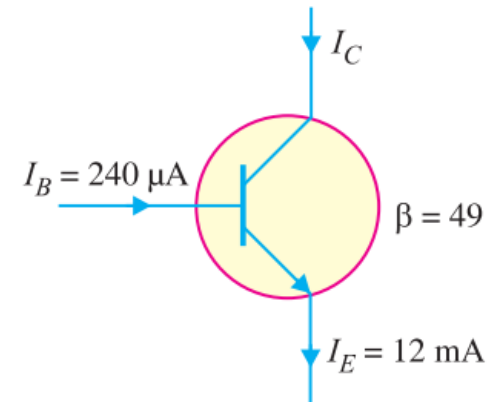
$$\text{Also } I_C = \beta I_B = 49 \times 240 \text{ }\mu\text{A} = \mathbf{11.76 \text{ mA}}$$



TRANSISTOR CONNECTION

Example 9:


For a transistor, $\beta = 45$ and voltage drop across $1k\Omega$ which is connected in the collector circuit is 1 volt. Find the base current for common emitter connection.

Solution:

$$I_C = \frac{1V}{1k\Omega} = 1 \text{ mA}$$

Now
$$\beta = \frac{I_C}{I_B}$$
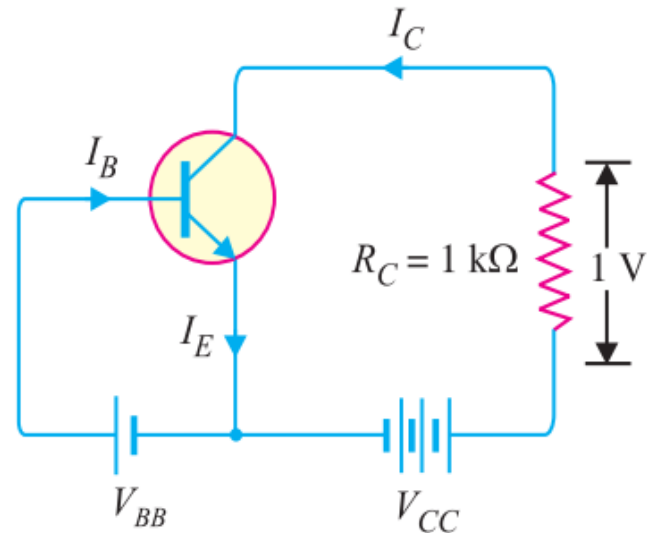
$$\therefore I_B = \frac{I_C}{\beta} = \frac{1}{45} = 0.022 \text{ mA}$$




TRANSISTOR CONNECTION

Review Questions

1. A transistor is connected in common emitter (CE) configuration in which collector supply is 8V and the voltage drop across resistance R_C connected in the collector circuit is 0.5V. The value of $R_C = 800\ \Omega$. If $\alpha = 0.96$, determine :

(i) collector-emitter voltage


(ii) base current

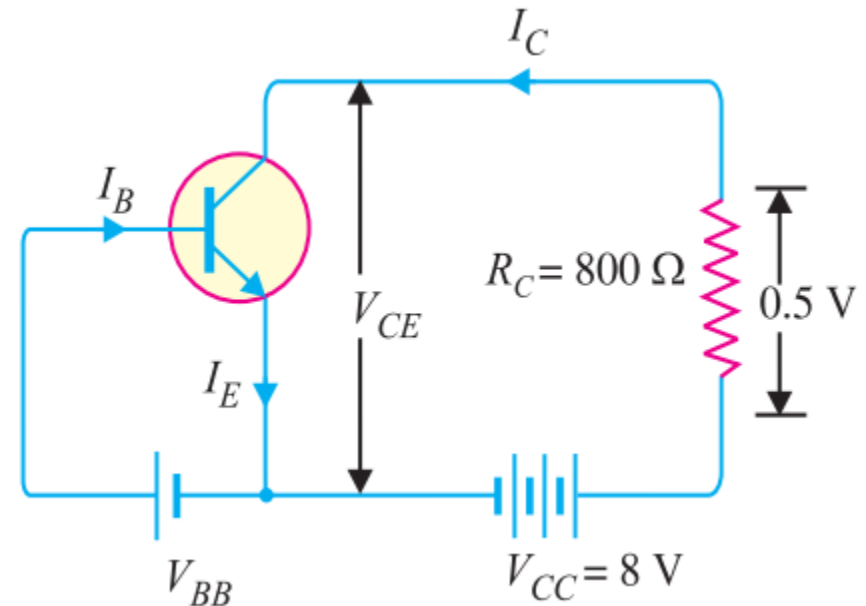

TRANSISTOR CONNECTION

Review Questions

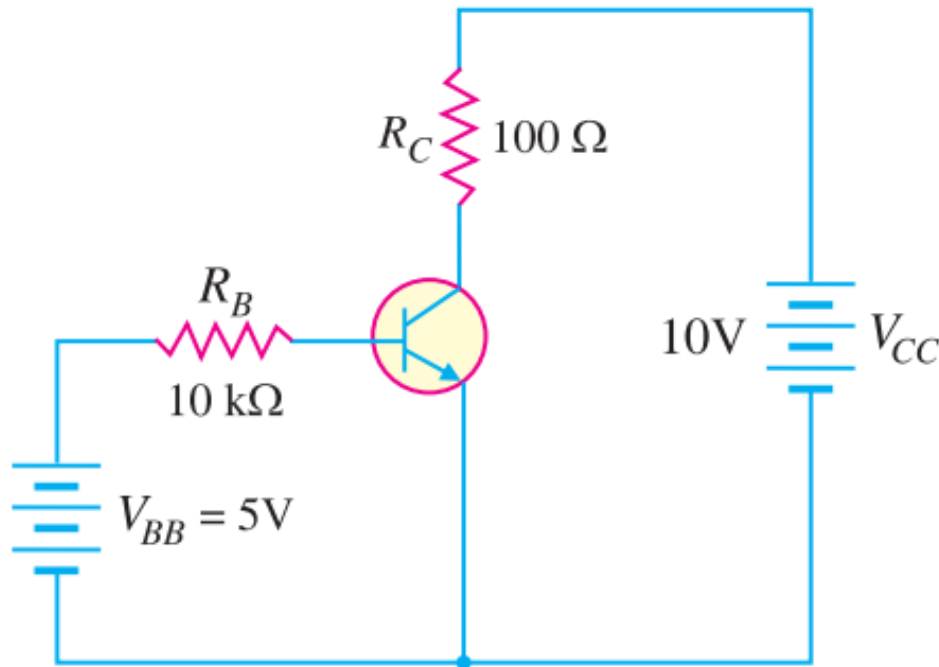2. Determine V_{CB} in the transistor circuit shown in Fig. The transistor is of silicon and has $\beta = 150$.



TRANSISTOR CONNECTION



Review Questions

- 3. In a transistor, $I_B = 68 \mu\text{A}$, $I_E = 30 \text{ mA}$ and $\beta = 440$. Determine the α rating of the transistor. Then determine the value of I_C using both the α rating and β rating of the transistor.*
 - 4. A transistor has the following ratings : $I_C (\text{max}) = 500 \text{ mA}$ and $\beta_{\text{max}} = 300$. Determine the maximum allowable value of I_B for the device.*
 - 5. What is the significance of arrow in the transistor symbol ?*
 - 6. Why is collector wider than emitter and base ?*
 - 7. Why is collector current slightly less than emitter current ?*
 - 8. Why is base made thin ?*
- 

TRANSISTOR CONNECTION

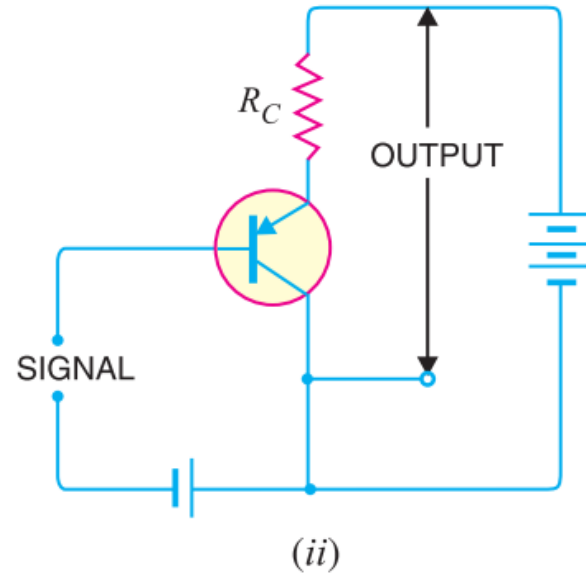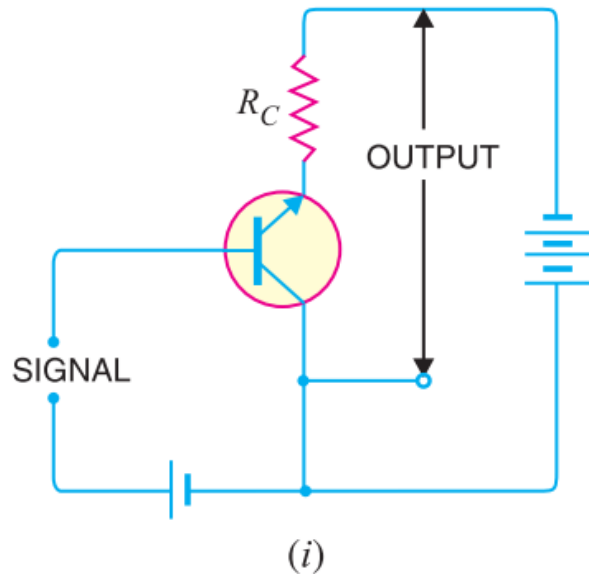3) Common Collector Connection

- The collector is common to both the input and output sides of the configuration.
- Input is applied between base and collector while output is taken between the emitter and collector.



TRANSISTOR CONNECTION

3) Common Collector Connection

□ Current amplification factor (γ)

- The ratio of change in emitter current (ΔI_E) to the change in base current (ΔI_B) is known as current amplification factor in common collector (CC) arrangement.

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

- Input current is the base current I_B and output current is the emitter current I_E .
- Current gain is same as in the common emitter circuit as $\Delta I_E \approx \Delta I_C$
- However, its voltage gain is always less than 1.

TRANSISTOR CONNECTION

3) Common Collector Connection

□ Relation between γ and α

$$\gamma = \frac{\Delta I_E}{\Delta I_B} \text{ and } \alpha = \frac{\Delta I_C}{\Delta I_E}$$

Now

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

$$\gamma = \frac{\frac{\Delta I_E}{\Delta I_E}}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{1}{1 - \alpha}$$

$$\gamma = \frac{1}{1 - \alpha}$$




COMMONLY USED TRANSISTOR CONNECTION

- Out of the three transistor connections, the **common emitter circuit** is the most efficient.
- It is used in about 90% to 95% of all transistor applications.
- The main reasons for the widespread use of this circuit arrangement are :
 - High current gain- range from 20 to 500
 - High voltage and power gain-due to high current gain
 - Moderate output to input impedance ratio- about 50



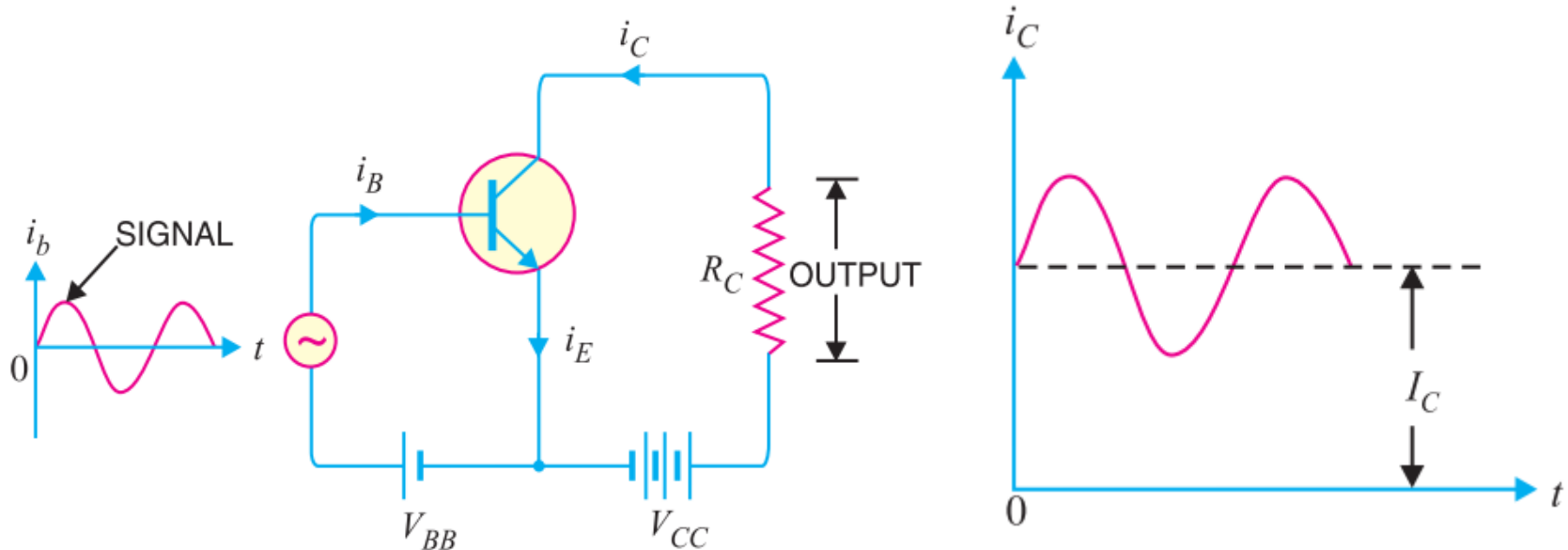TRANSISTOR AS AN AMPLIFIER IN CE ARRANGEMENT



- This is the common emitter npn amplifier circuit.
- A battery V_{BB} is connected in the input circuit in addition to the signal voltage.
- This d.c voltage is known as *bias voltage* and its magnitude is such that it always keeps the emitter-base junction **forward biased** regardless of the polarity of the signal source.

TRANSISTOR AS AN AMPLIFIER IN CE ARRANGEMENT

Operation

- During the positive half-cycle of the signal, the forward bias across the emitter-base junction is increased.
 - Therefore, more electrons flow from the emitter to the collector via the base.
 - This causes an increase in collector current.
 - The increased collector current produces a greater voltage drop across the collector load resistance R_C
 - However, during the negative half-cycle of the signal, the forward bias across emitter-base junction is decreased.
 - Therefore, collector current decreases. This results in the decreased output voltage (in the opposite direction).
 - Hence, an amplified output is obtained across the load.
- 

NEXT SESSION ...BJT BIAS CIRCUITS

