

DIGITAL ELECTRONICS

ET 8301

Monday, January 13, 2025

Mr. Cuthbert J. Karawa

Lecture 07

Sequential logic circuits

College of Information and Communication Technology (CoICT)


Department Of Electronics And Telecommunications Engineering.

Introduction

- Engineers classify logic circuits into two groups. We have already worked with **Combination logic circuits** using **AND**, **OR**, and **NOT** gates.
- The other group of circuits is classified as **Sequential logic circuits**. Sequential circuits involve **timing** and **memory devices**.
- The basic building block for combinational logic circuits is the **logic gate**.
- The basic building block for sequential logic circuits is the **flip-flop (FF)**.

Introduction

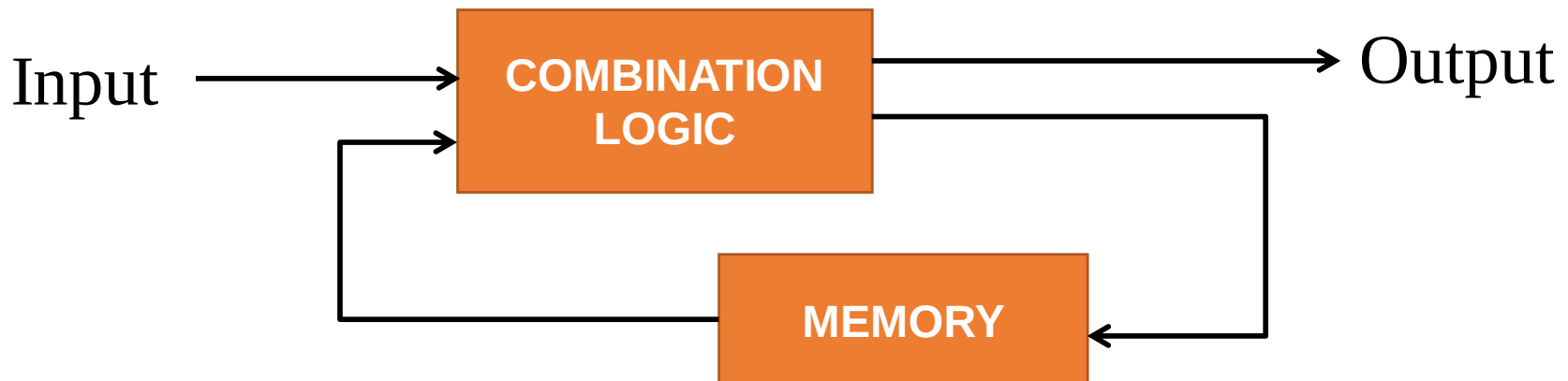- The logic circuits whose outputs at any instant of time depend on the present inputs as well as on the past outputs are called ***sequential circuits***.
- In sequential circuits, the output signals are **feedback to the input side**.
- A block diagram of a sequential circuit is shown in



Introduction


- Sequential circuits are classified broadly into **synchronous sequential circuits** and **asynchronous sequential circuits**.
- Synchronous sequential circuits are controlled by a **master clock**.
- While the operation of asynchronous sequential circuits are **not controlled by any clock pulses**. The **output change immediately to a change in input**.

Introduction

- Flip-flop is the **basic memory element in sequential circuits**.
- A flip-flop can store a **1** or a **0** indefinitely.
- We are going to cover several types of flip-flop circuits.
- Also will **wire flip-flops** together. Flip-flops are wired to form other sequential circuits such as **counters**, **shift registers**, and **various memory** devices.

Basic Bistable Element

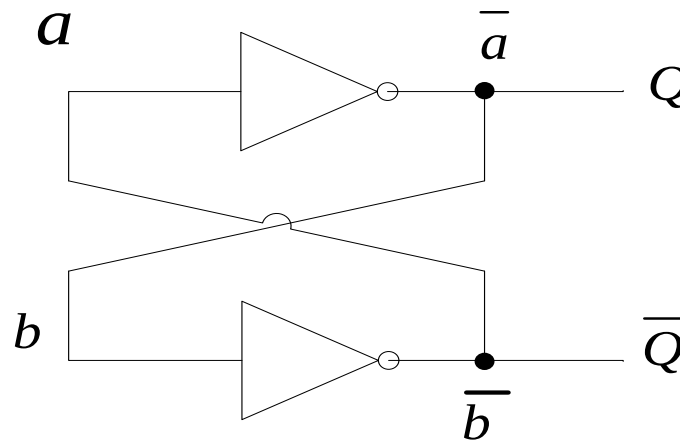- A circuit which indefinitely store a 1 or 0 is called a ***basic bistable element***.



Basic Bistable Element

- A **flip-flop** is a bistable circuit with input lines.
- The flip-flop remains in one of its two stable states until power is **switched off** or **until an input signal triggers** a change in state.
- A flip-flop is said to be **set or preset** when an input forced it to store a **1** and it is said to be **reset or cleared** when an input signal causes the flip-flop to store a **0**.

Basic Bistable Element


- Flip-flops are **synchronous** bistable devices, also known as **bistable multivibrators**.
- It **synchronous** because the output changes state only at a specified point (**leading or trailing edge**) on the triggering input called the **clock (CLK)** which is designated as a **control input**, C; that is, changes in the output occur in synchronization with the clock.
- Flip-flops are **edge-triggered or edge-sensitive**.

Basic Bistable Element

- A **latch** is a class of flip-flops whose output responds **immediately** to appropriate changes in the input in **spite of the presence of an enable or clock input**(asynchronous bistable devices).
- There are several types of latches based on types of **inputs** and **enable** lines.
- Latch are similar to flip-flops because they are bistable devices.
- The **main difference** between latches and flip-flops is in the **method used for changing state**.


The R-S Flip-Flop

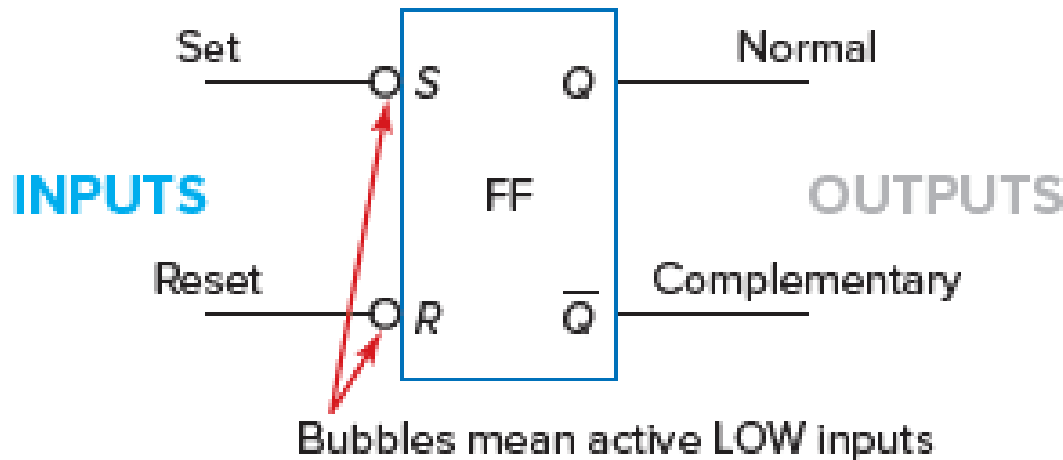- The logic symbol for the R-S flip-flop is shown below




- Notice that the **R-S** flip-flop has **two inputs**, labeled **S** and **R**. The **two outputs** are labeled Q and $\bar{Q}$ (say "not Q " or " Q not").
- In flip-flops the outputs are **always opposite**, or **complementary**. In other words, if output $Q = 1$, then output $\bar{Q} = 0$, and so on.

The R-S Flip-Flop

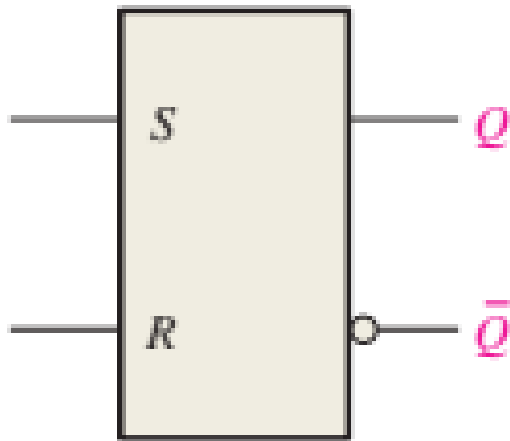

Active-HIGH input S-R Flip-Flop

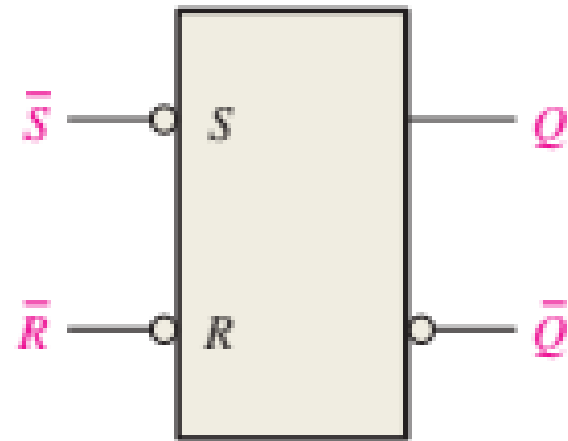

Active-LOW input S-R Flip-Flop

The R-S Flip-Flop

- The R-S flip-flop symbol shown above labels the outputs as **normal** and **complementary**.
- The letters S and R at the left of the R-S flip-flop symbol are often referred to as the **set** and **reset** inputs.
- The inputs are active LOW (see bubble).
- The **R-S flip-flop** may also be referred to as an **R-S latch**.
- The term "**latch**" refers to its use as a temporary memory device. A latch such as the R-S flip-flop in Figure above can **hold one bit of information**.

The R-S Flip-Flop

- The truth table for **active low** R-S flip-flop with details the operation are shown below

Truth Table A

Mode of operation	Inputs		Outputs		Effect on output Q
	S	R	Q	$\bar{Q}$	
Prohibited	0	0	1	1	Prohibited: Do not use
Set	0	1	1	0	For setting Q to 1
Reset	1	0	0	1	For resetting Q to 0
Hold	1	1	Q	$\bar{Q}$	Depends on previous state

OR

Truth Table B

Inputs		Outputs		Comments
$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$	
1	1	NC	NC	No change. Latch remains in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition

The R-S Flip-Flop

- From table A when the S and R inputs are **both 0**, both outputs go to a logical **1**. This is called a **prohibited state** for the flip-flop and is **not used**.
- The second line of the truth table shows that when input **S is 0** and **R is 1**, the Q output is **set** to logical **1**. This is called the **set condition**.
- The third line shows that when input **R is 0** and **S is 1**, output Q is **reset** (cleared) to **0**. This is called the **reset condition**.
- The fourth line in the truth table shows both **inputs (R and S) at 1**. This is the **idle or at rest condition** and leaves Q and $\bar{Q}$ in their previous complementary states. This is called the **hold condition**.

The R-S Flip-Flop


- From truth table , it may be observed that it takes a **logical 0 to activate the set** (set Q to 1).
- It also takes a **logical 0 to activate the reset**, or clear (clear Q to 0).
- Because it takes **a logical 0 to enable, or activate**, the flip-flop, the logic symbol in figure above is active low flipflop and has **invert bubbles at the R and S** inputs.
- These invert bubbles indicate that the set and reset inputs are activated by a logical 0.

The R-S Flip-Flop

- From truth table , it may be observed that it takes a **logical 0 to activate the set** (set Q to 1).
- It also takes a **logical 0 to activate the reset**, or clear (clear Q to 0).
- Because it takes **a logical 0 to enable, or activate**, the flip-flop, the logic symbol in figure above is active low flipflop and has **invert bubbles at the R and S** inputs.
- These invert bubbles indicate that the set and reset inputs are activated by a logical 0.

The R-S Flip-Flop

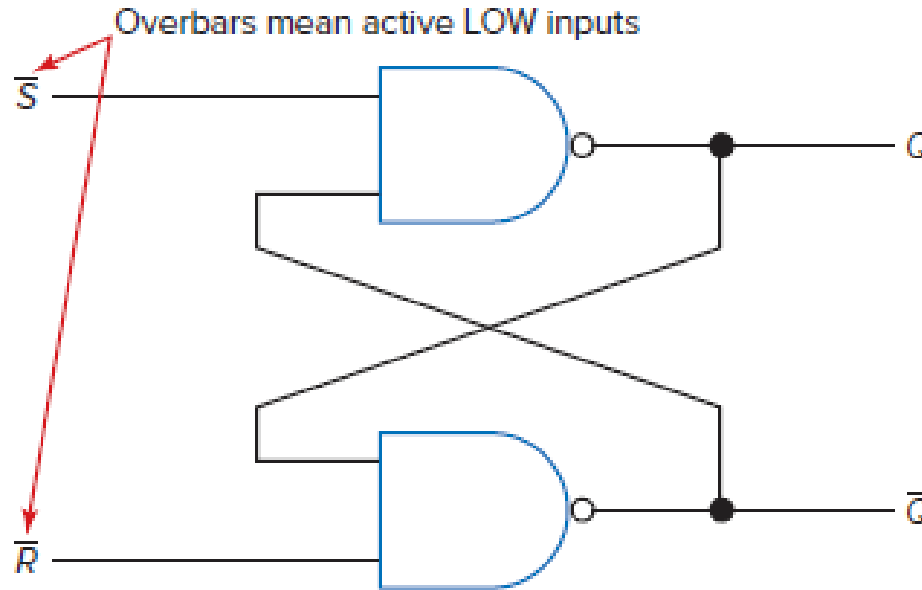- R-S flip-flops can be purchased in an IC package, or they can be wired from logic gates, as shown in figure below




- The NAND gates in figure above form an R-S flip-flop. This NAND-gate R-S flip-flop operates according to the truth table.

The R-S Flip-Flop

- Technically, the R-S flip-flop in figure above might be referred to as an **$\bar{R}$ - $\bar{S}$ flipflop** or **$\bar{R}$ - $\bar{S}$ latch**.
- The overbars above the R and S mean these are **active LOW inputs**.
- Many times **timing diagrams, or waveforms**, are given for sequential logic circuits.
- These diagrams show the voltage level and timing between inputs and outputs and are similar to what you would observe on an **oscilloscope**.
- The horizontal distance is **time**, and the vertical distance is **voltage**.

The R-S Flip-Flop

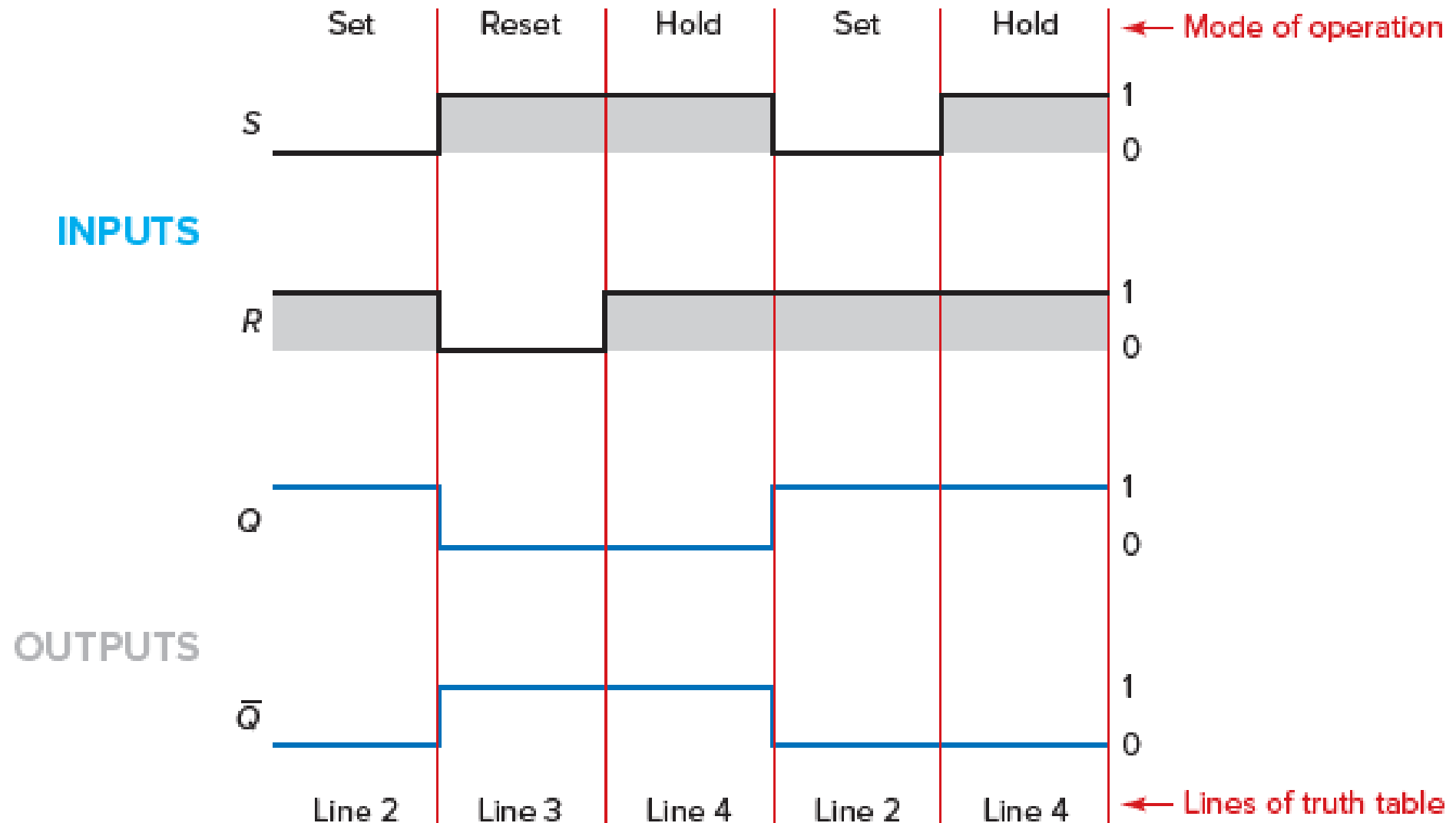


The R-S Flip-Flop

- There are three types of **multivibrators (MVs)**. They are **the monostable MV**, **the astable MV**, and **the bistable multivibrator**.
- The R-S flip-flop is one of several bistable MVs. The R-S flip-flop is most commonly known as a latch and is listed under this heading in IC latch catalogs.

The R-S Flip-Flop

- A **latch** is a fundamental binary memory device for holding data.
- Latches are *commonly used at the output of a digital device to hold the data until the next device is ready to receive the input.*
- Latches are commonly organized into groups of 4-bits, 8-bits, or more into registers.
- An 8-bit register would be a group of eight latches holding a **byte of information.**
- R-S flip-flops were also used for switch debouncing.

The R-S Flip-Flop

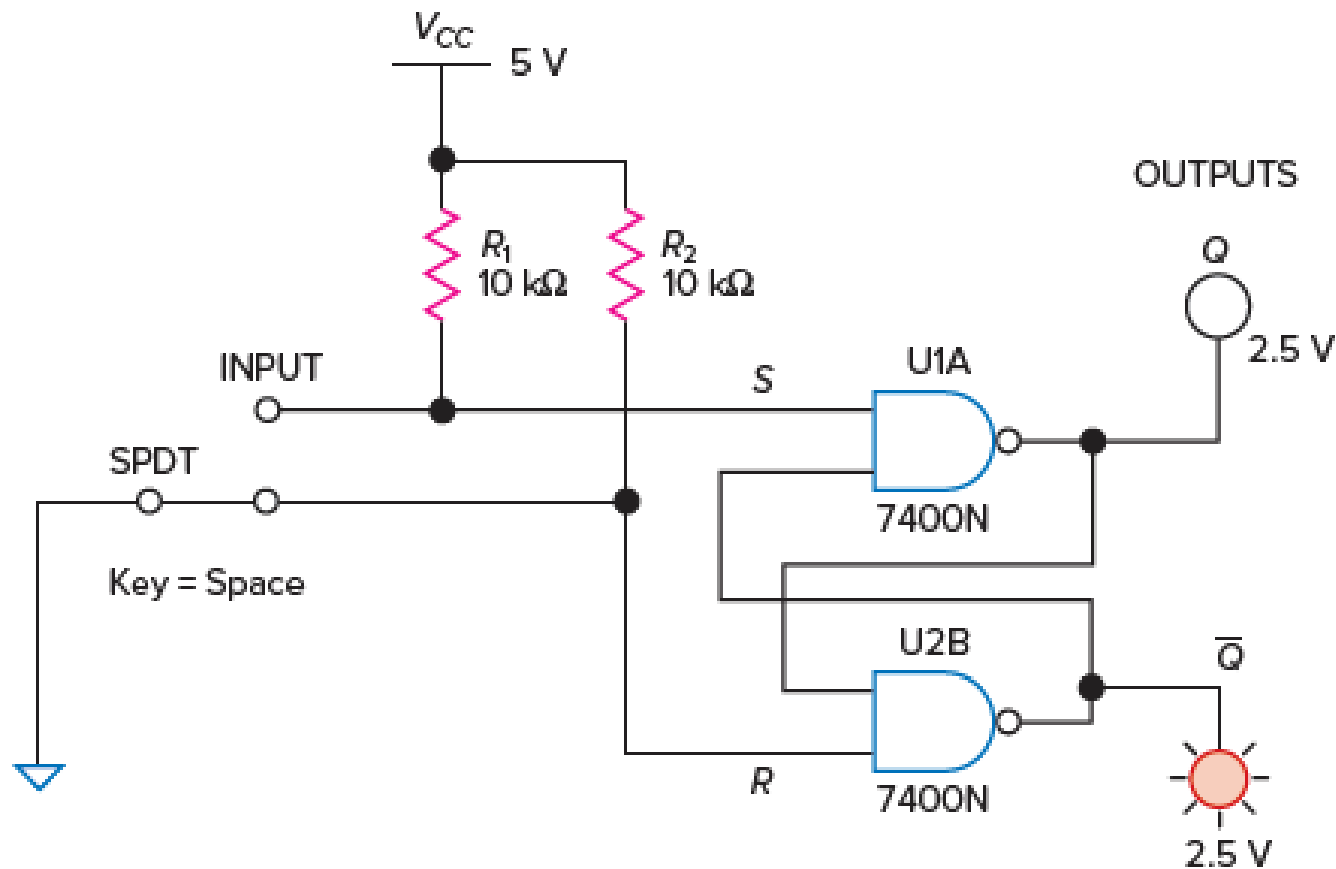

➤ R-S flip-flop in an SPDT switch debouncing circuit.

The R-S Flip-Flop




**DID YOU
KNOW?**

- The logic symbol and truth table for the R-S flip-flop?
- The four modes of operation for the R-S flip-flop?

The Clocked R-S Flip-Flop

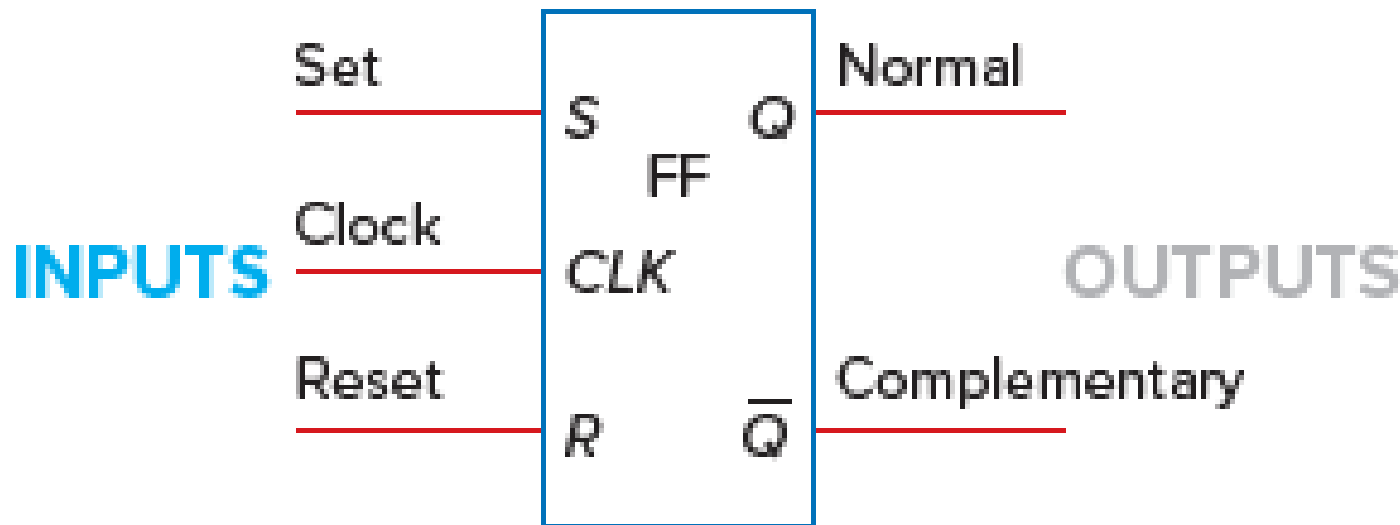
- The logic symbol for a **clocked R-S flip-flop** is shown in figure below



- You can observe that it looks almost like an R-S flip-flop except that **it has one extra input labeled CLK (for clock)**.

The Clocked R-S Flip-Flop

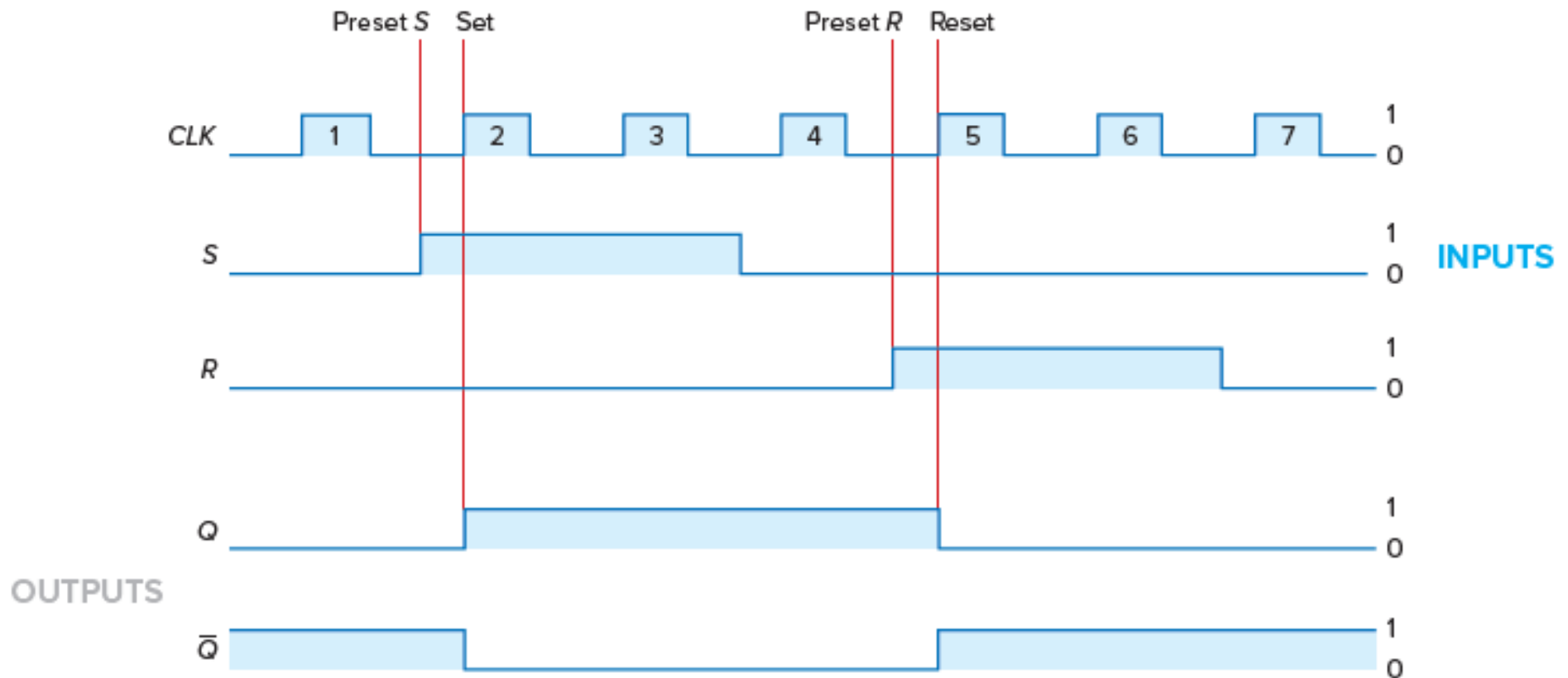- The operation of the clocked R-S flip-flop is detailed in figure below where the CLK input is at the top of the diagram as shown below.



The Clocked R-S Flip-Flop

- Notice that the **clock pulse (1)** has no effect on output Q with inputs S and R in the 0 position (Active High). The flip-flop is in the idle, or hold, mode during clock pulse 1.
- At the preset S position, the S (set) input is moved to 1, but **output Q is not yet set to 1**.
- The rising edge of **clock pulse 2** permits **Q to go to 1**. Pulses 3 and 4 have no effect on output Q. During pulse 3, the flip-flop is in its set mode, and during pulse 4, it is in its hold mode.

The Clocked R-S Flip-Flop


- Next, **input R is preset to 1**. On the rising edge of clock pulse 5, **the Q output is reset (or cleared) to 0**.
- The flip-flop is in the reset mode during both clock pulses 5 and 6.
- The flip-flop is in its hold mode during **clock pulse 7**; therefore, the normal output (Q) remains at **0**.

The Clocked R-S Flip-Flop

- Notice that the outputs of the clocked R-S flip-flop change **only on a clock pulse**.
- We say that this flip-flop **operates synchronously**; it operates in step with the clock.
- Synchronous operation is very important in most digital circuits, where each step must happen in an exact order.
- Another characteristic of the clocked R-S flip-flop is that once it is set or reset, **it stays that way even if you change some inputs**.
- This is a **memory characteristic**, which is extremely valuable in many digital circuits.

The Clocked R-S Flip-Flop

➤ The truth table for the Clocked R-S Flip-Flop.

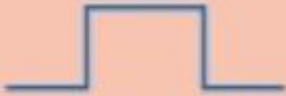
Mode of operation	INPUTS			OUTPUTS		
	<i>CLK</i>	<i>S</i>	<i>R</i>	<i>Q</i>	$\bar{Q}$	Effect on output <i>Q</i>
Hold		0	0	No change		No change
Reset		0	1	0	1	Reset or cleared to 0
Set		1	0	1	0	Set to 1
Prohibited		1	1	1	1	Prohibited—do not use

The Clocked R-S Flip-Flop

- From the truth table above for the clocked R-S flip-flop. You can notice that only the **top three lines** of the truth table are usable; **the bottom line is prohibited and not used**.
- You can also observe that the R and S inputs to the clocked R-S flip-flop are **active HIGH inputs**.
- That is, it takes a **HIGH** on input **S** while **R = 0** to cause output **Q to be set to 1**.

The Clocked R-S Flip-Flop

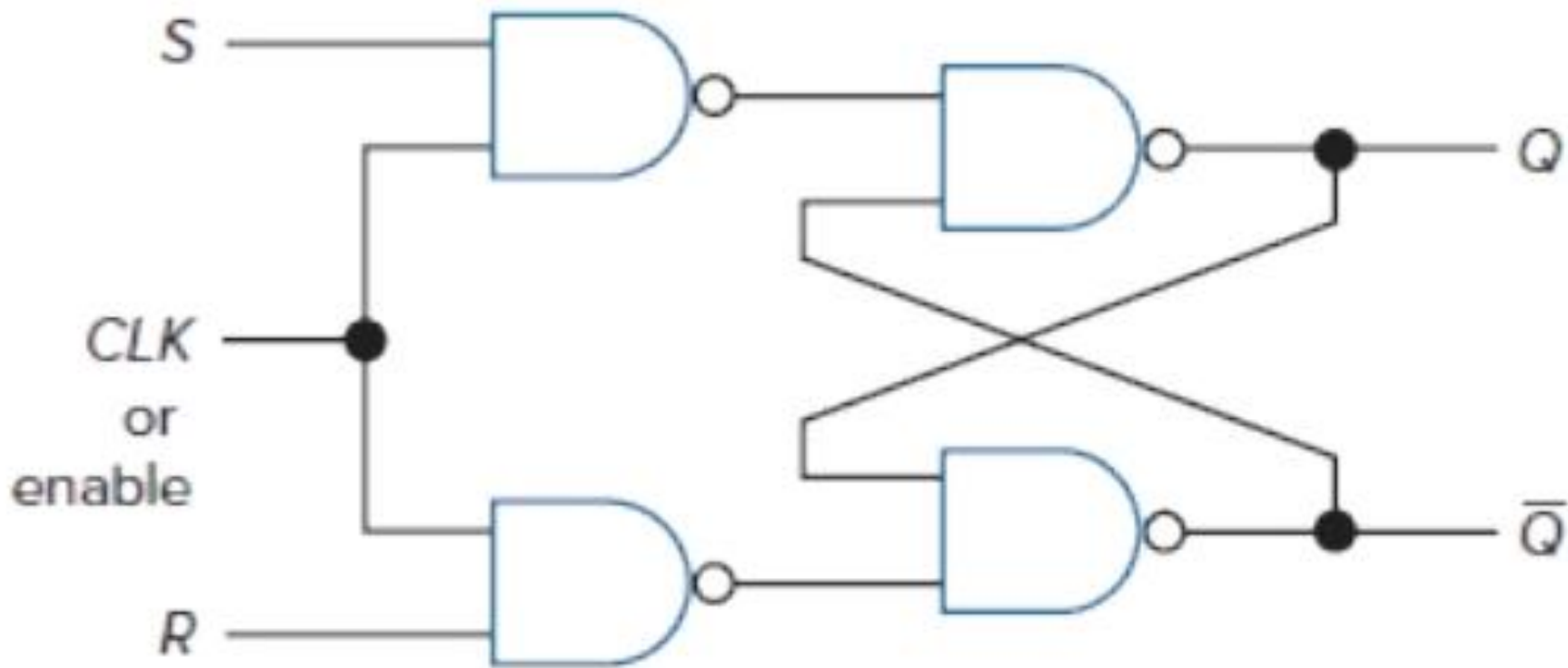- The **wiring diagram** of a clocked R-S flip-flop




The Clocked R-S Flip-Flop

- You can notice that two **NAND gates** have been **added to the inputs** of the R-S flip-flop to add the clocked feature.
- The CLK input may be labeled with a **C or E** for enable by various manufacturers.
- It is **important to remember** that the memory characteristics exhibited by flip-flops are among the fundamental reasons why digital technology has become so widely used in modern electronic products.

The D Flip-Flop

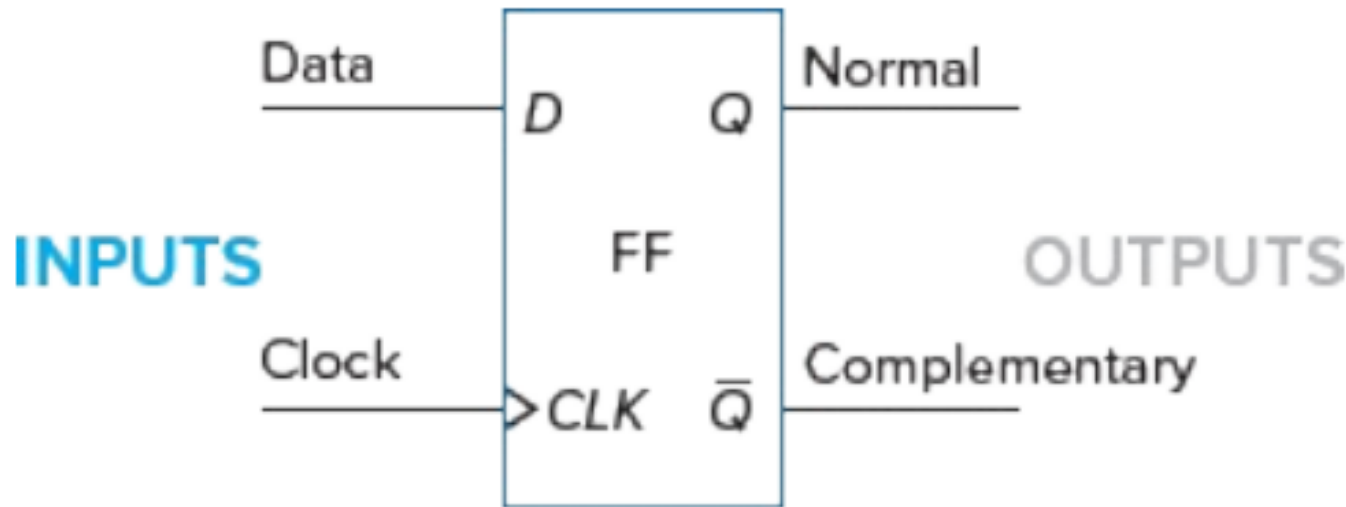- The logic symbol for the D flip-flop is shown in figure below.



- It has only **one data input (D)** and a **clock input (CLK)**. The **outputs** are labeled **Q** and **$\bar{Q}$** .


The D Flip-Flop

- The D flip-flop is often called a **delay flip-flop**.
- The word delay describes **what happens to the data, or information**, at input D.
- The data (a **0 or 1**) at input D is **delayed one clock pulse** from getting to output Q.
- The truth table for the D flip-flop is shown below

Input	Output
D	Q^{n+1}
0	0
1	1


The D Flip-Flop

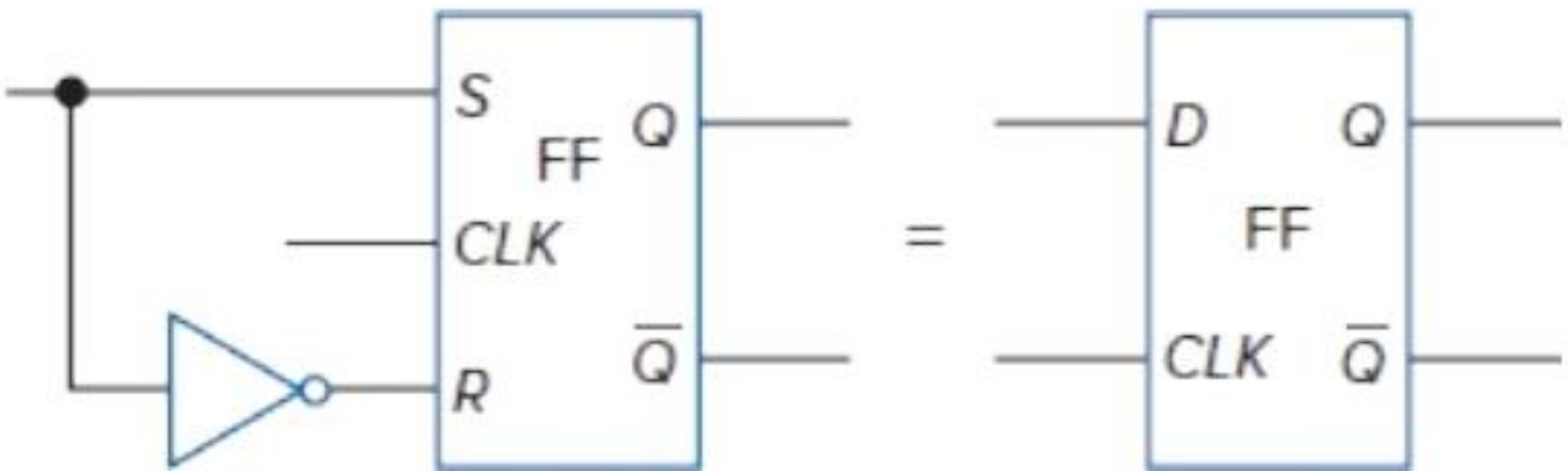- Notice that output Q follows **input D** after one clock pulse (see Q^{n+1} column).
- A **D flip-flop may be formed from a clocked R-S flip-flop** by adding an inverter, as shown in figure below



The D Flip-Flop

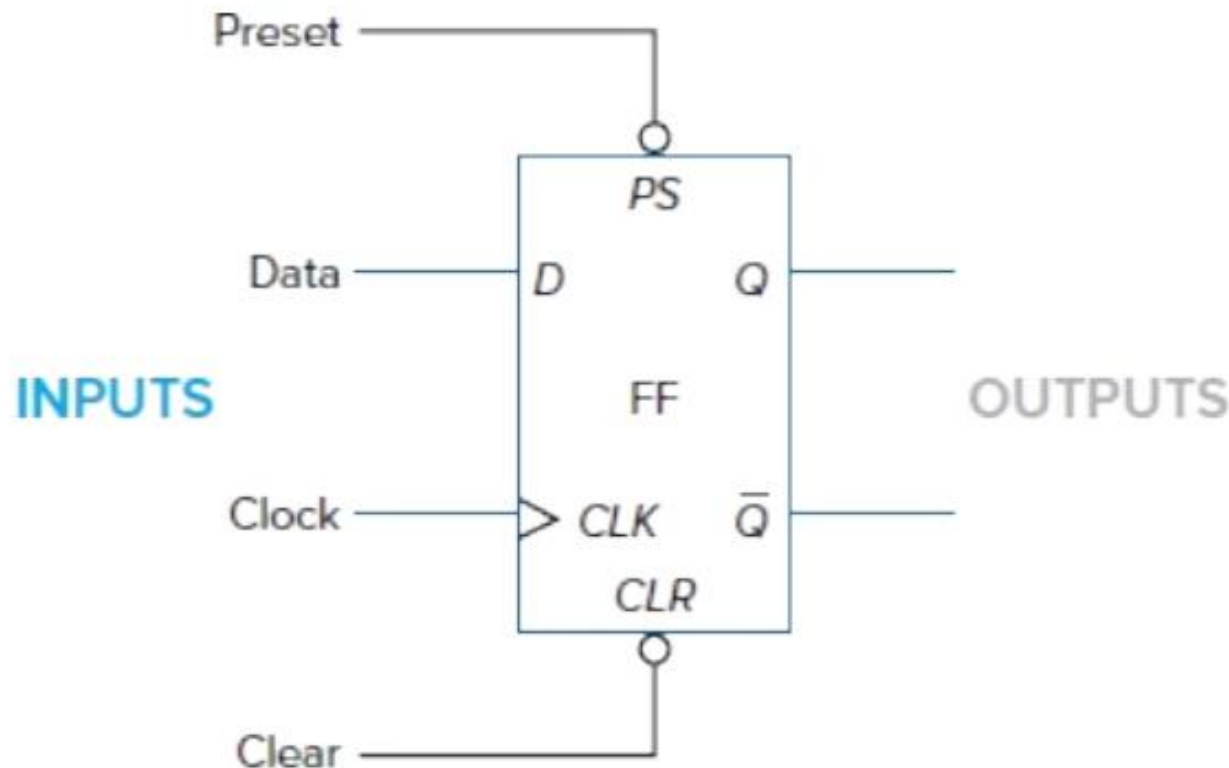- More commonly we will use a D flip-flop contained in an IC. The figure below shows a typical commercial D flip-flop.



The D Flip-Flop

- Two extra inputs [**PS (preset)** and **CLR (clear)**] have been added to the D flip-flop in Figure above
- The **PS input** sets **output Q to 1** when enabled by a logical **0**. The **CLR input clears output Q to 0** when enabled by a logical **0**.
- The **PS** and **CLR** inputs will **override** the D and CLK inputs.
- Note the addition of a **small triangle** on the CLK input of the IC symbol means the flip-flop is **edge-triggered**.

The D Flip-Flop

- During synchronous operation, edge triggering means the bit of data present at input D is transferred to output Q on the **positive edge (LOW-to-HIGH transition)** of the clock pulse.
- The **7474 D flip-flop IC** is said to be positive-edge triggered.

The D Flip-Flop

➤ The truth table for 7474 D flip-flop.

Mode of operation	INPUTS				OUTPUTS	
	Asynchronous		Synchronous			
	<i>PS</i>	<i>CLR</i>	<i>CLK</i>	<i>D</i>	<i>Q</i>	$\bar{Q}$
Asynchronous set	0	1	X	X	1	0
Asynchronous reset	1	0	X	X	0	1
Prohibited	0	0	X	X	1	1
Set	1	1	↑	1	1	0
Reset	1	1	↑	0	0	1

0 = LOW

1 = HIGH

X = Irrelevant

↑ = LOW-to-HIGH transition of clock pulse

The D Flip-Flop

- **Remember** that the asynchronous (not synchronous) inputs (PS and CLR) **override the synchronous inputs**.
- The asynchronous inputs are in control of the D flip-flop in the first three lines of the truth table above.
- The synchronous inputs (D and CLK) are irrelevant as shown by the **X's** on the truth table.
- The **prohibited condition, line 3** on the truth table, should be **avoided**.
- With **both asynchronous inputs disabled** (PS = 1 and CLR = 1), the D flip-flop can be set and reset using the **D** and **CLK** inputs.

The D Flip-Flop

- The last two lines of the truth table use a clock pulse to transfer data from **input D to output Q** of the flip-flop. Being in step with the clock, this is called **synchronous operation**.
- **Note** that this flipflop uses the **LOW-to-HIGH** transition of the clock pulse to **transfer data from input D to output Q**.


The D Flip-Flop

- **D flip-flops** are sequential logic devices, which are widely used **temporary memory devices**.
- D flip-flops are wired together to form **shift registers** and **storage registers**. These registers are commonly used in digital systems.
- **Remember** that the D flip-flop **delays the input data from reaching the output** (Q) until a clock pulse has taken place.
- Due to this delay, it is called a **delay flip-flop**. D flip-flops are sometimes also called **data flipflops** or **D-type latches**.
- D flip-flops are available in both **TTL** and **CMOS** IC form.

The D Flip-Flop


➤ Example

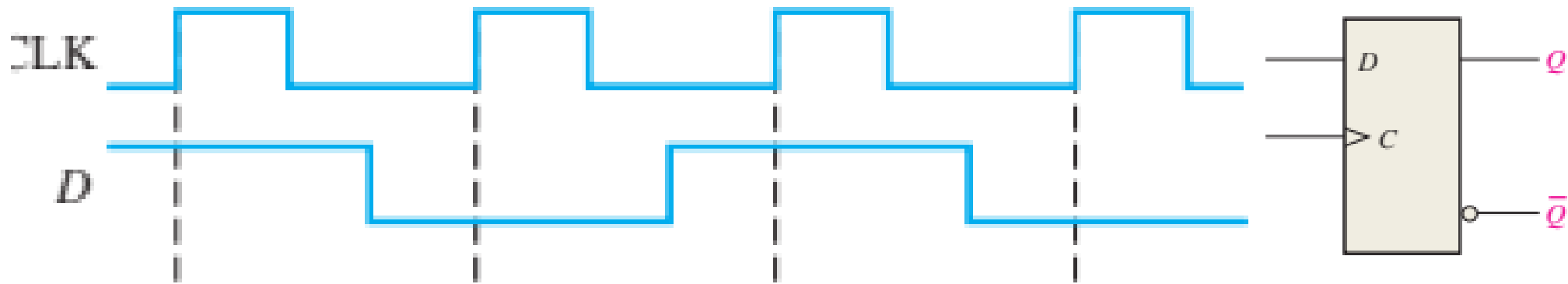Given the waveforms in Figure below for the ***D* input** and the clock, determine the ***Q output*** and **$\bar{Q}$ output** waveform if the flip-flop starts out RESET.



The J-K Flip-Flop

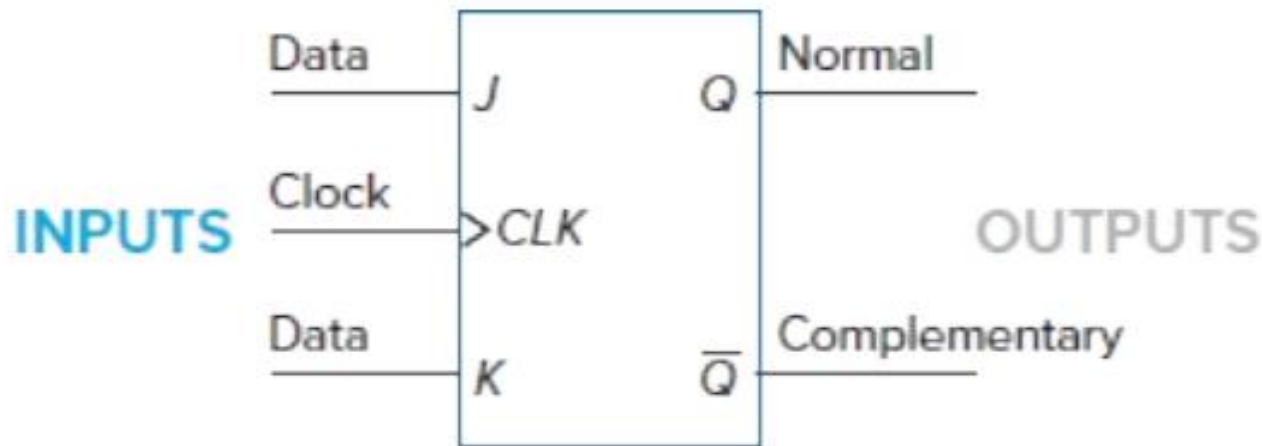- The J-K flip-flop has the features of **all the other types of flip-flops**.
- The logic symbol for the J-K flip-flop is illustrated in figure below.



- The inputs labeled **J** and **K** are **the data inputs**. The input labeled **CLK** is the **clock input**.
- **Outputs Q** and **$\bar{Q}$** are the usual **normal** and **complementary** outputs on a flip-flop.

The J-K Flip-Flop

➤ A truth table for the J-K flip-flop is shown below


Mode of operation	INPUTS			OUTPUTS		
	<i>CLK</i>	<i>J</i>	<i>K</i>	<i>Q</i>	$\bar{Q}$	Effect on output <i>Q</i>
Hold		0	0	No change		No change—disable
Reset		0	1	0	1	Reset or cleared to 0
Set		1	0	1	0	Set to 1
Toggle		1	1	Toggle		Changes to opposite state

The J-K Flip-Flop

- When the **J** and **K** inputs are both **0**, the flip-flop is in the **hold mode**.
- In the hold mode, **the data inputs have no effect on the outputs**. The outputs “**hold**” the last data present.
- From the truth table **lines 2** and **3** show that the **reset** and **set** conditions for the **Q output**.
- **Line 4** illustrates the useful **toggle position of the J-K flip-flop**.
- When both data inputs **J** and **K** are at **1**, repeated clock pulses cause the output to **turn off-on-off-on-off-on**, and so forth.
- This off-on action is like a toggle switch and is called **toggling**.

The J-K Flip-Flop

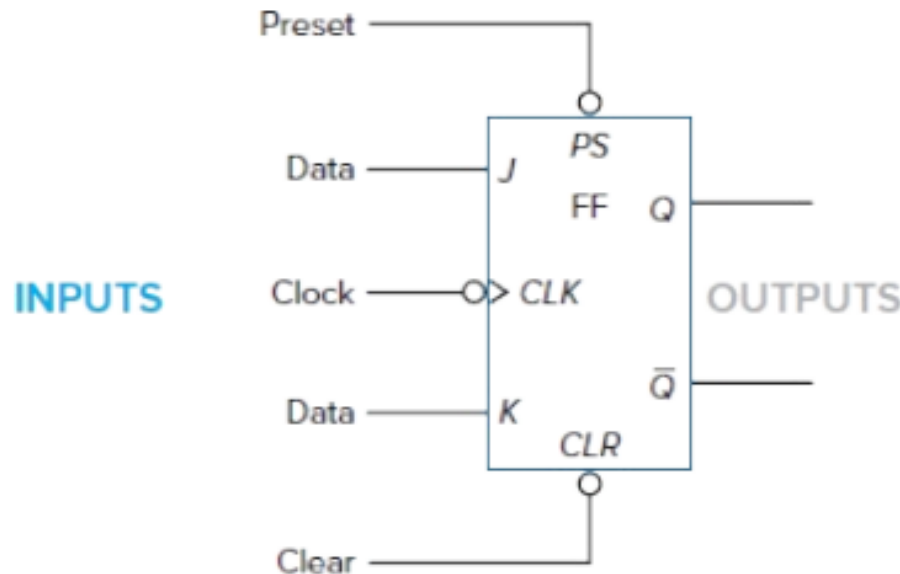- The logic symbol for the commercial **7476 TTL J-K flip-flop** is shown in figure below



- The **two asynchronous inputs** were added to the symbol two (**preset** and **clear**).
- The **synchronous inputs** are the J and K data and clock inputs.

The J-K Flip-Flop

- The **customary normal (Q)** and **complementary $\bar{Q}$** outputs. A detailed truth table for the commercial 7476 J-K flip-flop is shown in figure below

Mode of operation	INPUTS					OUTPUTS	
	Asynchronous		Synchronous				
	<i>PS</i>	<i>CLR</i>	<i>CLK</i>	<i>J</i>	<i>K</i>	<i>Q</i>	$\bar{Q}$
Asynchronous set	0	1	X	X	X	1	0
Asynchronous reset	1	0	X	X	X	0	1
Prohibited	0	0	X	X	X	1	1
Hold	1	1		0	0	No change	
Reset	1	1		0	1	0	1
Set	1	1		1	0	1	0
Toggle	1	1		1	1	Opposite state	

0 = LOW

1 = HIGH

X = Irrelevant

 = Positive clock pulse

The J-K Flip-Flop

- You can recall the **asynchronous inputs** (such as **PS** and **CLR**) from the D Flipflop section **always will override synchronous inputs**.
- The asynchronous inputs are **activated in the first three lines** of the truth table.
- The synchronous inputs are irrelevant (overridden) in the first three lines as shown in the truth table above.
- The **prohibited state** occurs when both asynchronous inputs are activated at the same time. The prohibited state is **not useful** and should be **avoided**.

The J-K Flip-Flop

- When both **asynchronous inputs** (**PS** and **CLR**) are **disabled** with a 1, the synchronous inputs can be **activated**.
- The bottom four lines of the truth table above detail the **hold**, **reset**, **set**, and **toggle modes** of operation for the 7476 J-K flip-flop.
- **Note that** the 7476 J-K flip-flop uses the entire pulse to **transfer** data from the **J** and **K data inputs** to the **Q** and $\bar{Q}$ outputs.
- J-K flip-flops are used in many digital circuits. You will use the J-K flip-flop especially in **counters**.
- Counters are found in almost every digital system.


The J-K Flip-Flop

In **summary**,

- the J-K flip-flop is considered the “**universal**” **flip-flop**. Its unique feature is the toggle mode of operation so useful in designing counters.
- When the J-K flip-flop is wired for use only in the **toggle mode**, it is commonly called a **T flip-flop**.

The T Flip-Flop

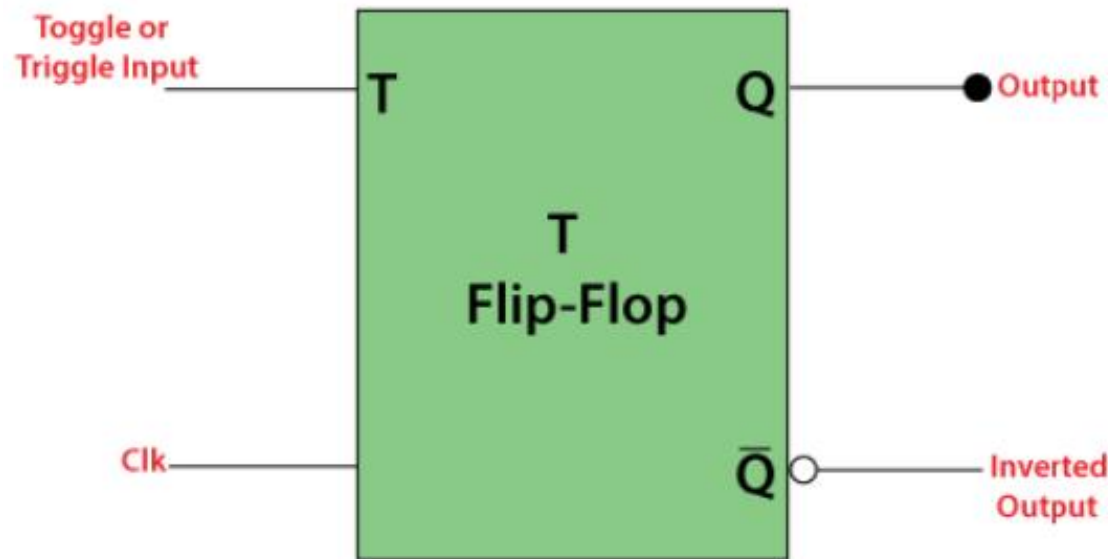- The **T flip-flop** has the features like all the other types of flip-flops.
- The logic symbol for the T flip-flop is illustrated in figure below.



The T Flip-Flop

- In T flip flop, "**T**" defines the term "**Toggle**".
- In **T Flip Flop**, we provide only a single input called "**Toggle**" or "**Trigger**" input to avoid an intermediate state occurrence.
- It work as a **Toggle switch**.
- The **next output state is changed** with the complement of the **present state output**. This process is known as "**Toggling**".


The T Flip-Flop

➤ Truth Table of T Flip Flop is shown in table below

	Previous		Next	
T	Q	Q'	Q	Q'
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1



Tutorials

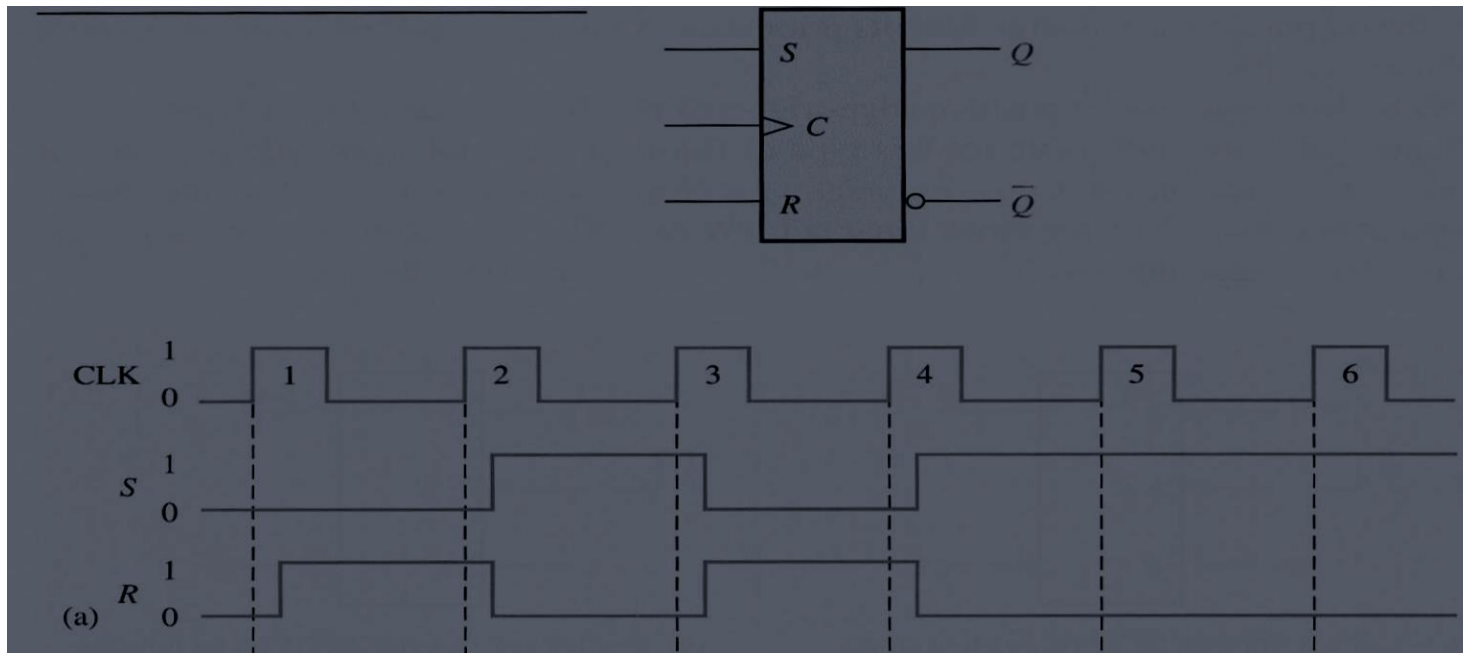- Determine the Q and $\bar{Q}$ output waveforms of the flip-flop in Fig 1 for S , R and CLK inputs. Assume that the positive triggered flip-flop is initially RESET



Tutorials

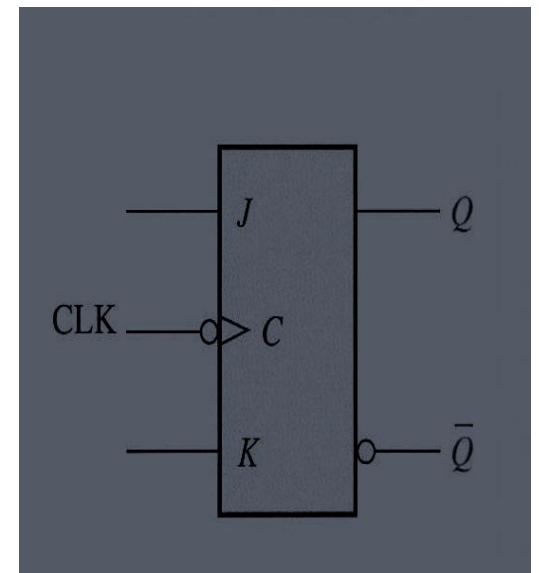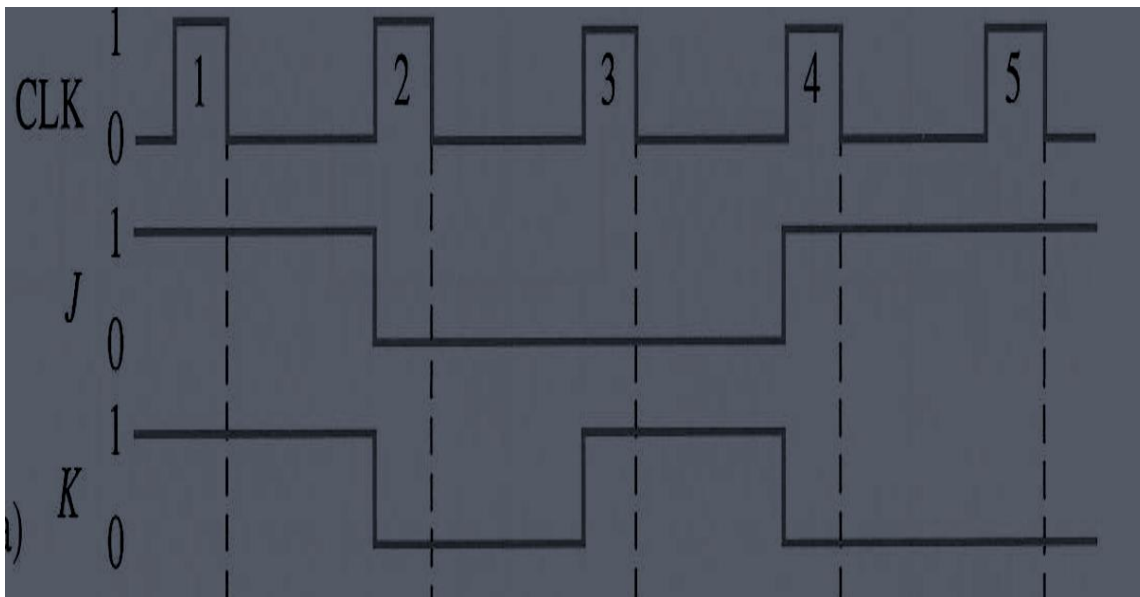- The waveforms of Fig are applied to the J, K and clock inputs as indicated. Determine the Q output assuming the flip-flop is initially RESET





Homework

- Read chapter 7 of Digital Fundamentals by Floyd
- Read more above Negative Edge triggering flipflop