

QUESTION ONE

Choose the most correct answer

- I. Which of the following is a characteristic of digital signals?
 - A. Continuous variation of signal amplitude
 - B. Represented using discrete levels or states
 - C. More susceptible to compared to analog signals
 - D. Difficult to store and using computers
- II. What is the main advantage of digital electronics over analog electronics?
 - A. Lower power consumption in all cases
 - B. Ability to handle high-frequency signals easily
 - C. Greater resistance to noise signal degradation
 - D. Easier design of high-p amplifiers
- III. Which component is most commonly associated with digital electronics?
 - A. Operational amplifiers
 - B. Resistors
 - C. Microprocessors
 - D. Transformers
- IV. In digital systems, a binary "1" typically represents which of the following?
 - A. A high voltage level
 - B. A low voltage level
 - C. A continuously varying signal
 - D. An undefined state
- V. Which of the following statements is true about analog signals?
 - A. They have discrete levels or steps for signal representation.
 - B. They are more suitable for long-distance transmission without degradation.
 - C. They can take any value within given range.
 - D. They are always represented in binary form.
- VI. In the 2's complement form, the binary number 01101101 is equal to the decimal number
 - A. -19
 - B. +109
 - C. +91
 - D. -109
- VII. The binary number for $F7C9_{16}$ is
 - A. 1111011110101001₂
 - B. 1111011111001001₂
 - C. 1110111110101001₂
 - D. 1111011010101001₂
- VIII. The BCD number for decimal 473 is
 - A. 111011010
 - B. 110001110011
 - C. 010001110011
 - D. 010011110011
- IX. The Boolean expression $X = (A + B)(C + D)$ represents
 - A. Two ORs ANDed together
 - B. Two ANDs ORed together
 - C. A 4-input AND gate
 - D. A 4-input OR gate
- X. An example of a standard SOP expression is
 - A. $\bar{A}B + A\bar{B}C + AB\bar{D}$
 - B. $A\bar{B}C + A\bar{C}D$
 - C. $A\bar{B} + \bar{A}B + AB$
 - D. $A\bar{B}C\bar{D} + \bar{A}B + A$

QUESTION TWO

(10 Marks)

- i. Express -87 decimal number as an 8-bit number in the 1's complement form [03 Marks]

1000111
101000

REG No: _____

- ii. Convert 56 and 227 decimal numbers to binary and add using the 2's complement form [03 Marks]
- iii. Develop a circuit with inputs A, B, C, D where the output is **HIGH** if A is **HIGH**, or B, C , and D are all **HIGH**. [04 Marks]

(20 Marks)

QUESTION THREE

- i. Simplify the following Boolean expression using Boolean laws and rules
 $[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$
- ii. Use a Karnaugh map to find the minimum SOP form for the expression below
 $A + B\bar{C} + CD$
- iii. Use NAND gates to implement the following logic expression
 $\bar{A}B + CD + \overline{(A + B)}(ACD + \bar{B}E)$
- iv. Use NOR gates to implement the following logic expression
 $ABC\bar{D} + \bar{D}EF + A\bar{F}$

[05 Marks]

[05 Marks]

[05 Marks]

[05 Marks]

QUESTION ONE - ANSWER

I	II	III	IV	V	VI	VII	VIII	IX	X
B	C	A	A	C	B	B	E	A	C

TIME: 60 Minutes

DATE: 26th January, 2025


INSTRUCTIONS

1. Answer **ALL** questions.

QUESTION ONE

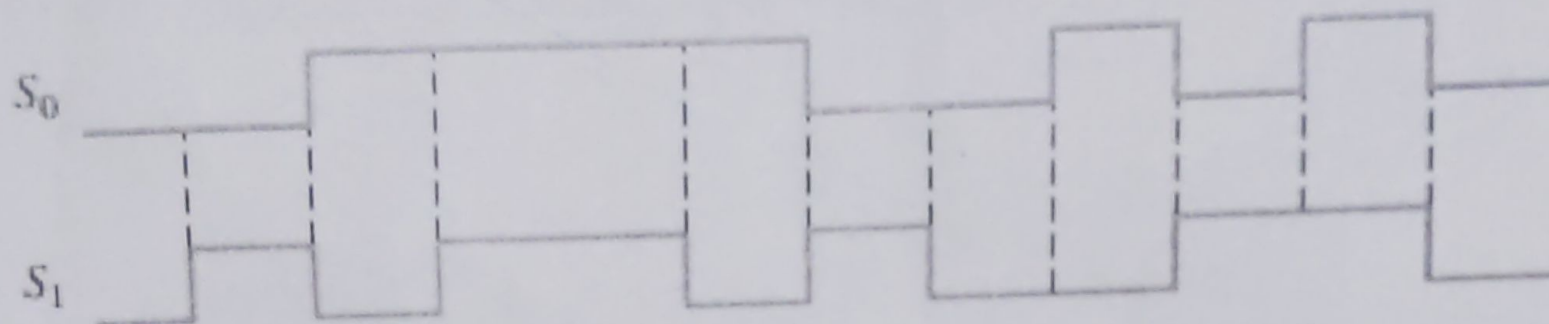(02.5 Marks)

If the data-select inputs to the 4 to 1 multiplexer are sequenced as shown by the waveforms in Figure below, determine the output waveform with the data inputs $D_0 = 1$, $D_1 = 0$, $D_2 = 0$, $D_3 = 1$.



QUESTION TWO

(02.5 Marks)

Convert the following SOP expression to an equivalent POS expression:

$$\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C + ABC$$

REG No: _____

(05 Marks)

QUESTION THREE

Determine the Q and $\bar{Q}$ output waveforms of the flip-flop in Figure A for the D and CLK inputs in Figure B, Assume that the positive edge-triggered flip-flop is initially RESET

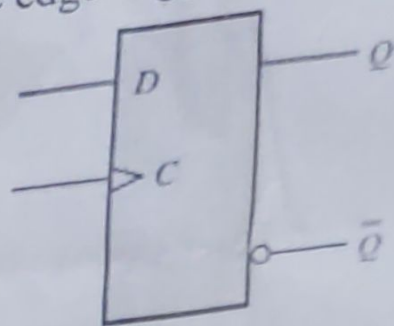


Figure A

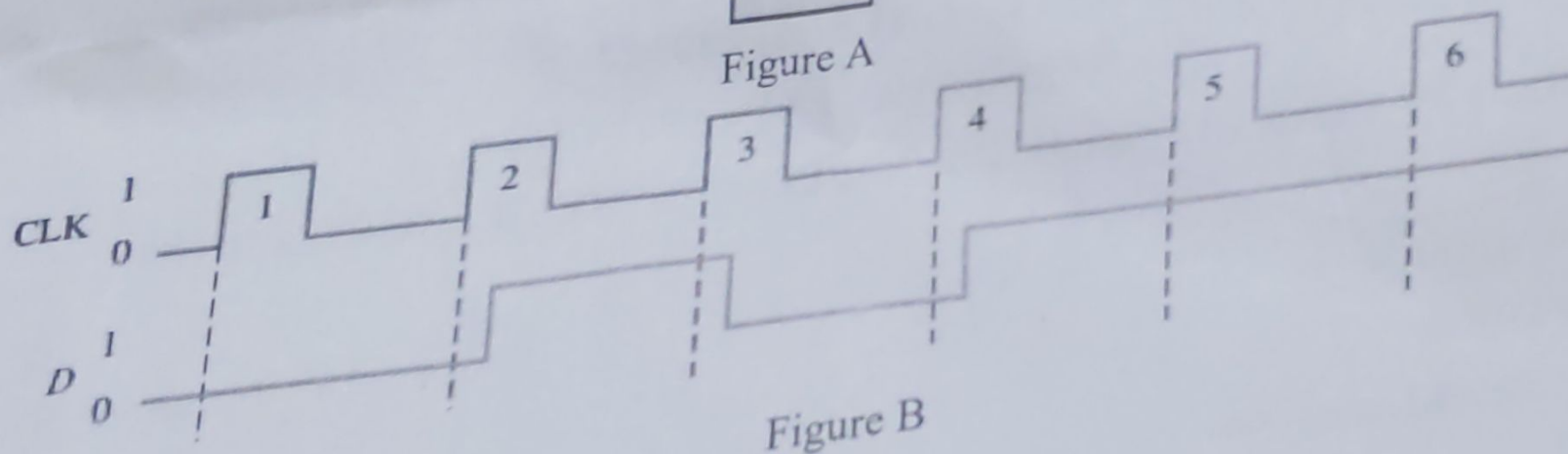


Figure B

(05 Marks)

QUESTION FOUR

Design a counter with the binary count sequence 1,2,5,7. Use D flip-flops.

	D_0	D_1	D_2	D_3
1	0	0	1	1
2	1	0	1	1
5	0	1	0	1
7	1	1	0	1

(0, 3, 4, 2)